
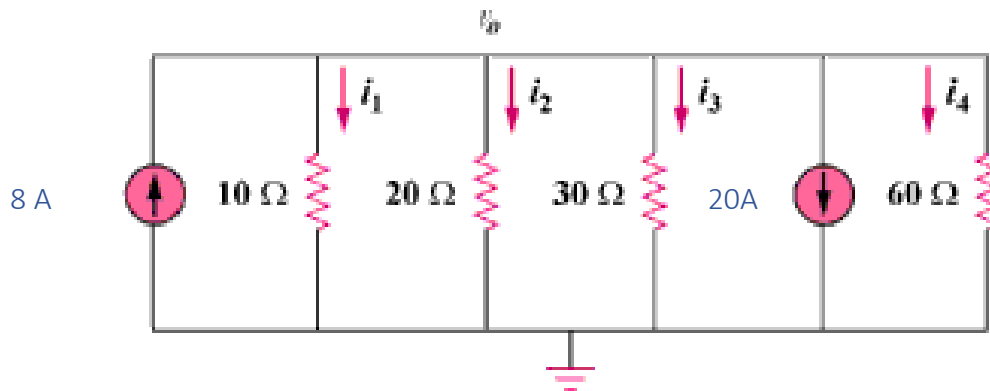


### Assignment problems: Chapter 3

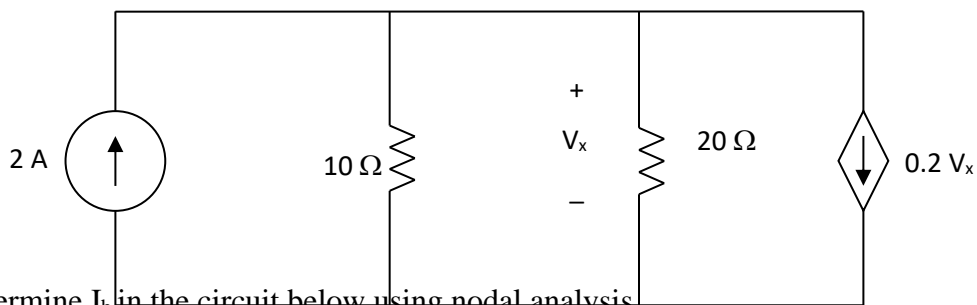
3.3 Find the currents  $i_1$  through  $i_4$  and the voltage  $v_o$  in the following circuit.




3.7: Apply nodal analysis to solve for  $V_x$  in the following circuit.



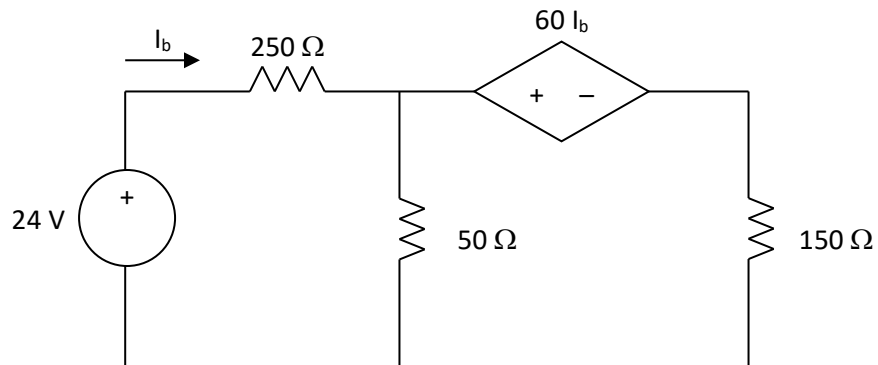
3.9: Determine  $I_b$  in the circuit below using nodal analysis.



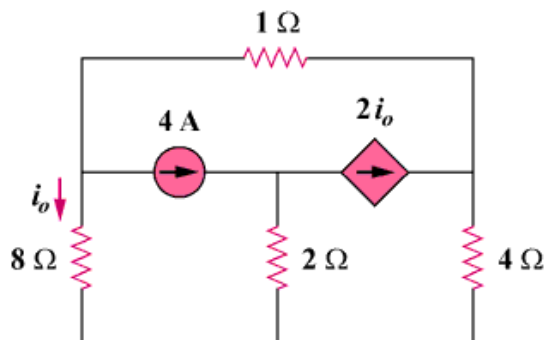
3.10: Find  $i_o$  in the following circuit.



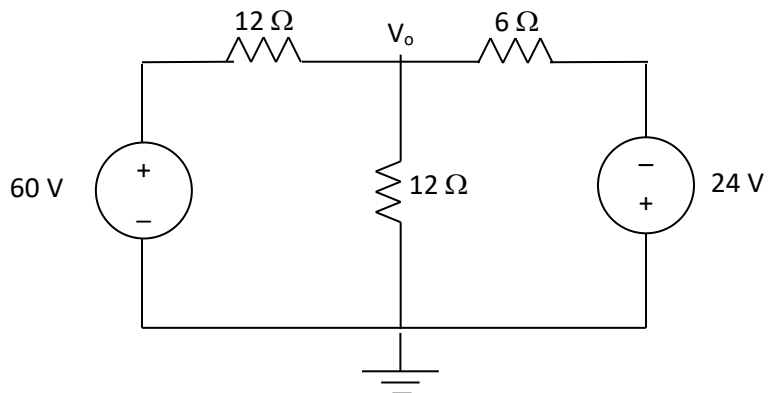
**3.11:** Find  $V_o$  and the power dissipated in all the resistors in the following circuit.



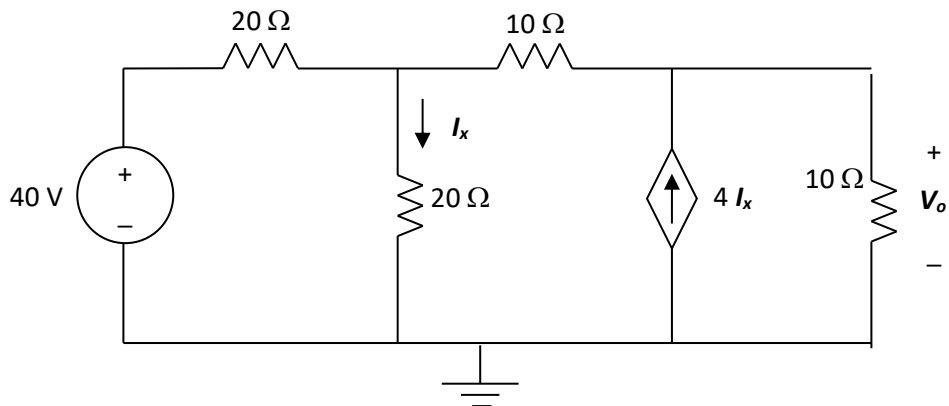
**3.12:** Using nodal analysis, determine  $V_o$  in the following circuit.



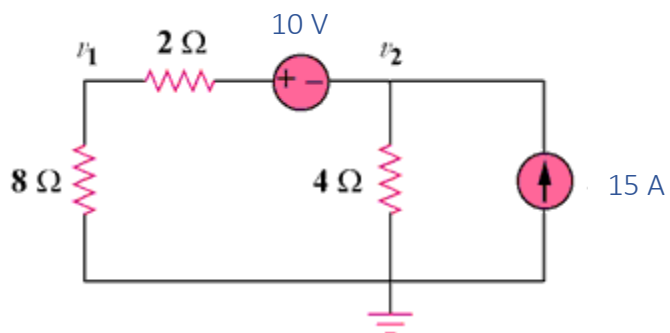
**3.13:** Calculate  $v_1$  and  $v_2$  in the following circuit, using nodal analysis.



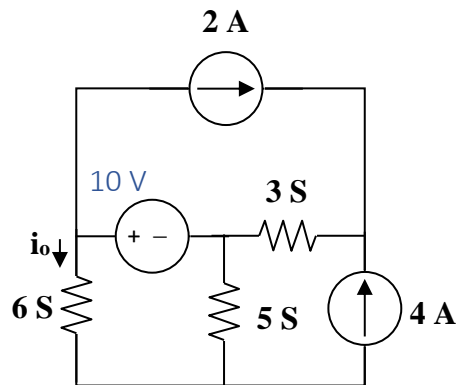
**3.15:** Apply nodal analysis to find  $i_o$  and the power dissipated in each resistor in the following circuit.



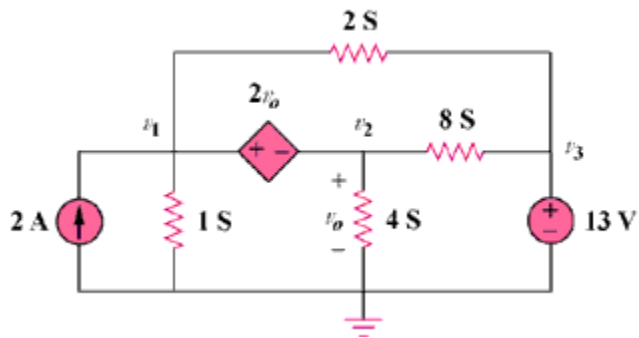
**3.16:** Determine voltages  $v_1$  through  $v_3$  in the following circuit, using nodal analysis.



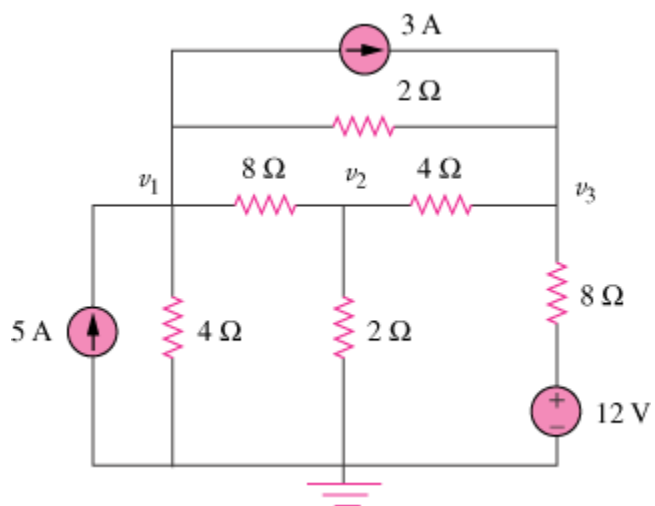
**3.19:** Use nodal analysis to find  $v_1$ ,  $v_2$ , and  $v_3$  in the following circuit.



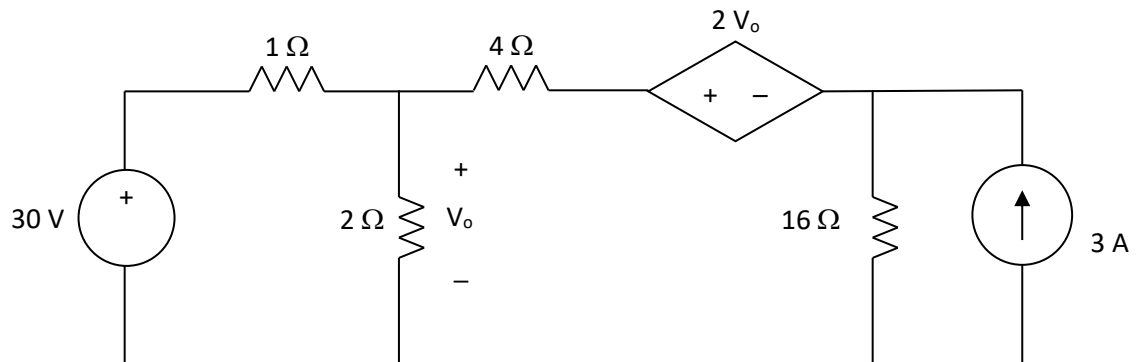
**3.23:** Use nodal analysis to find  $V_o$ .



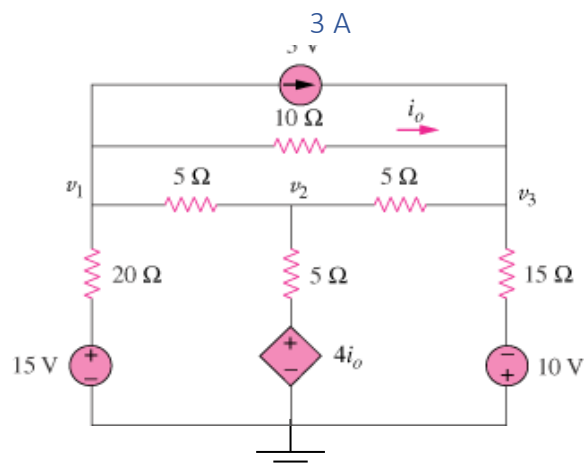
**3.26:** Calculate the node voltages  $v_1$ ,  $v_2$ , and  $v_3$ .




**3.31:** Find the node voltages.

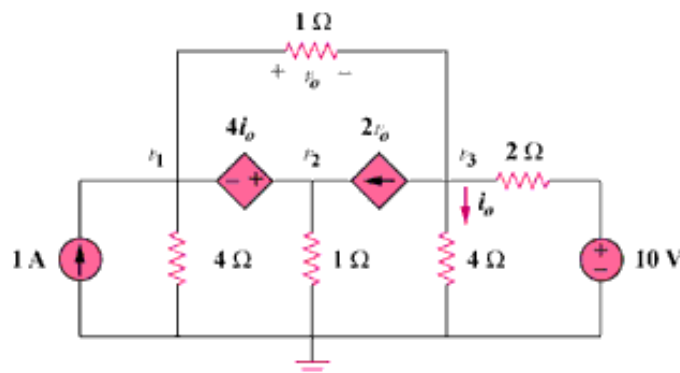

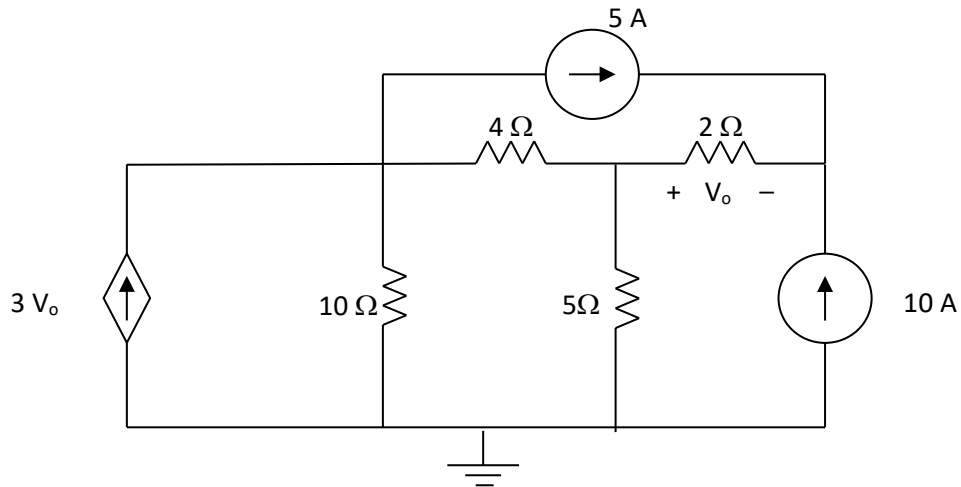**3.67:** Obtain the node-voltage equations and then solve for  $V_o$ .



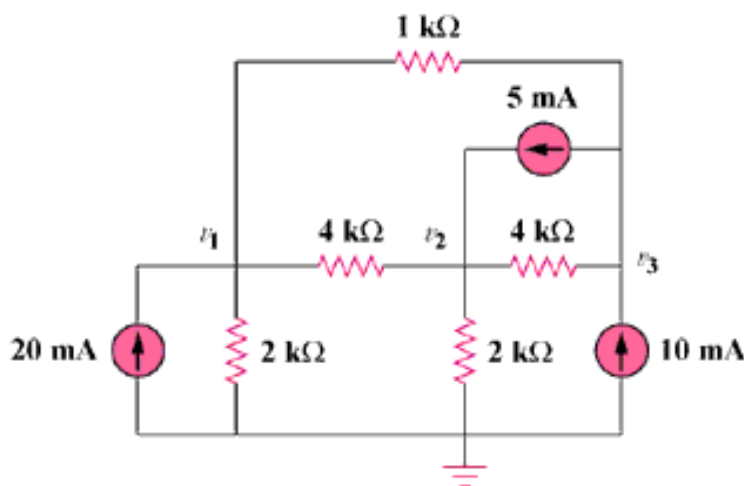**3.69:** Write the node voltage equations by inspection.



**3.77:** Solve for  $V_1$  and  $V_2$ .

