

BJT Amplifier Example

Design an Amp w/: $R_{in} \approx 10k\Omega$

$$R_o \approx 10k\Omega$$

$$|A_{voltage}| \approx 50 V/V$$


$$V_{cc} = 10V$$

$$\text{Assume } V_{BE(on)} = 0.7V$$

$$V_{CE(sat)} = 0.3V$$

$$\beta = 100$$


Given the requirements, let's use a CE:

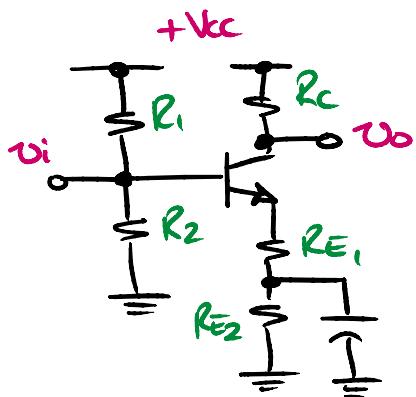

→ for bias current stability (i.e. insensitivity to β & temperature variations), the voltage across the emitter degen. shld be $> 3V_{BE}$

→ for a good swing set $V_c \approx \frac{1}{2}(V_{cc} + V_E)$


so:

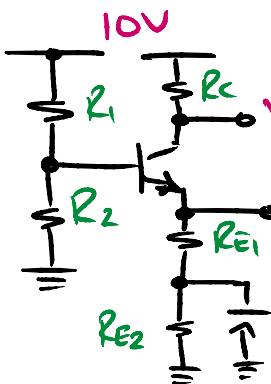

$$V_c = \frac{1}{2}(10 + 2.1 + 0.3) = 6.2V$$

accounting for $V_{CE(sat)}$

$$V_E = 3 \cdot 0.7 = 2.1V$$

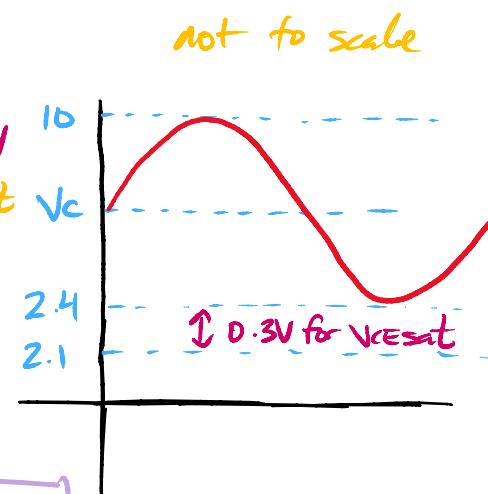


→ In a CE, $R_o = R_c \rightarrow$ set $R_c = 10k\Omega$

→ Therefore $I_C = \frac{10 - 6.2}{10} = 0.384mA$


$$I_C = \alpha I_E \rightarrow \beta = 100 \rightarrow \alpha = 0.99$$

$$I_E = 0.384mA$$

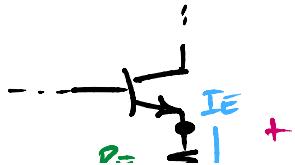


$$\rightarrow 2.1 = 0.384(R_{E1} + R_{E2})$$

$$10 - 0.384(R_{E1} + R_{E2})$$

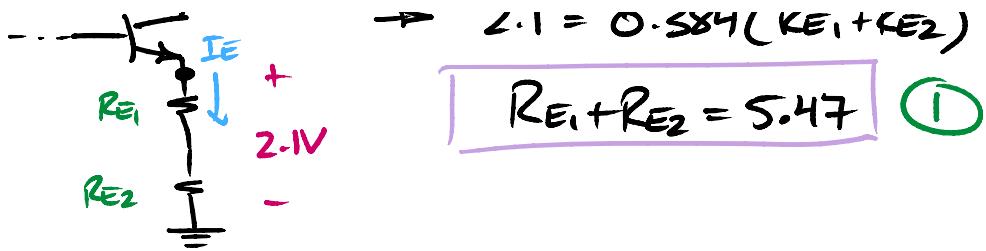

AC Analysis:

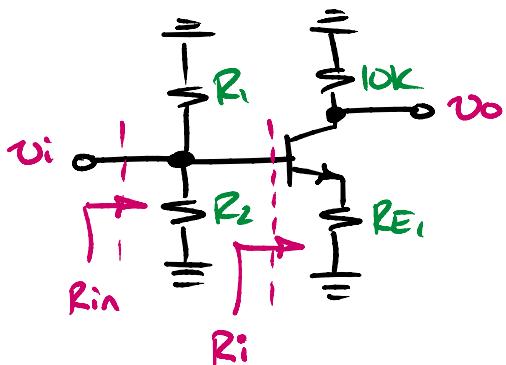

$$R_i = r_{pi} + (\beta + 1)R_{E1}$$

$$\Rightarrow g_m = 40I_c = 40(0.38)$$

$$g_m = 15.2 \mu\text{S}$$

$$\rightarrow A_{vo} = \frac{-g_m R_c}{1 + g_m R_{E1}} \Rightarrow SD = \frac{(15.2)(10)}{1 + (15.2)(R_{E1})}$$

$$\Rightarrow R_{E1} = 0.134 \text{ k}\Omega$$

FROM ①:

$$R_{E2} = 5.47 - 0.134 \Rightarrow R_{E2} = 5.34 \text{ k}\Omega$$

Since R_h should be $\geq 10\text{k}\Omega$;


$$R_{in} = R_1 // R_2 // R_i$$

$$\rightarrow R_i = \frac{\beta}{g_m} + (\beta + 1)R_{E1} = \frac{100}{15.2} + 10(0.134)$$

$$R_i = 20.1 \text{ k}\Omega$$

$$\frac{1}{10} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{20} \rightarrow R_1 // R_2 \geq \left(\frac{1}{10} - \frac{1}{20}\right)^{-1}$$


Let $R_1 // R_2 = 20\text{k}$;

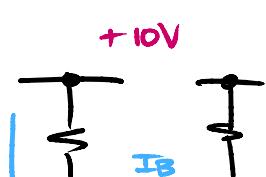

$$\rightarrow I_c = \beta I_B \rightarrow I_B = 0.0038 \text{ mA}$$

↳ assume $I_B \ll I$:
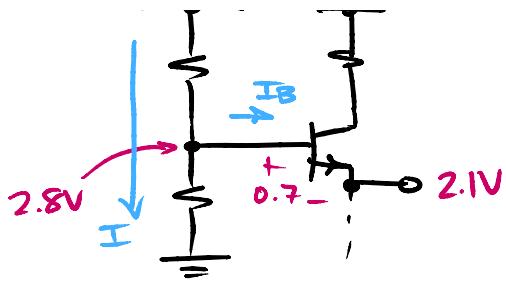
$$\text{Since } R_1 // R_2 = 20 \rightarrow \underline{R_1 R_2 = 20} \quad \textcircled{2}$$



Since $R_1 \parallel R_2 = 20 \rightarrow$

$$\frac{R_1 R_2}{R_1 + R_2} = 20 \quad (2)$$

Note: I is the current flowing in the divider, ignoring I_B .

Ignoring I_B : $2.8 \approx 10 \cdot \frac{R_2}{R_1 + R_2}$

$$\frac{R_1 + R_2}{R_2} = 3.57 \quad (3)$$

Solve (2) and (3);

$$R_1 = 71.4 \text{ k}\Omega$$


$$R_2 = 27.8 \text{ k}\Omega$$

Check I : $I \approx \frac{10}{71.4 + 27.8} = 0.1 \text{ mA} = 100 \mu\text{A}$

$\hookrightarrow I \gg I_B$, so our approximation is valid.

What if we want a lower output resistance, which most practical amps have?

Suppose $R_o = 0.1 \text{ k}\Omega$

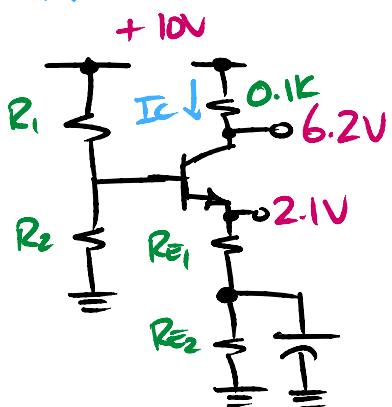

$$\rightarrow I_C = \frac{10 - 6.2}{0.1} = 38 \text{ mA}$$

\hookrightarrow stupid big.

$$\rightarrow R_{E1} + R_{E2} = \frac{2.1}{38 \cdot \frac{101}{100}} = 0.0547 \text{ k}\Omega$$

$$\rightarrow g_m = 40 \cdot 38 = 1520 \mu\text{S}$$

$$\rightarrow A_{v_o} = \frac{-g_m R_C}{1 + g_m R_{E1}} \rightarrow R_{E1} = 0.00134 \text{ k}\Omega$$

$$\rightarrow R_{in} = R_1 \parallel R_2 \parallel [r_{pi} + (B+1)R_{E1}]$$



$$R_{in} = \frac{100}{100 + 1520(1 + 38)} = 0.02 \text{ k}\Omega$$

$$R_{in} = R_1 \parallel R_2 \parallel L \left[\frac{1}{\pi} + (\beta+1) R_E \right]$$

$$R_i = \frac{100}{1520} + 10(0.00134) = 0.2k\Omega$$

↳ This means R_{in} cannot exceed $0.2k\Omega$, meaning we can't achieve our goal.

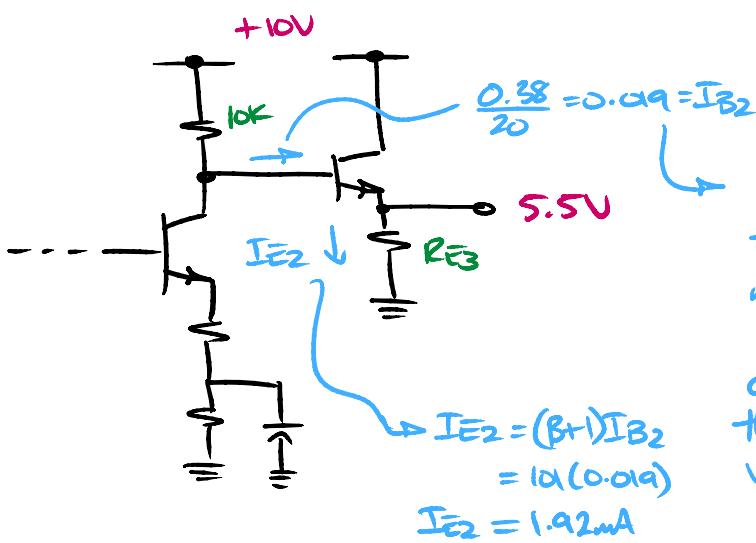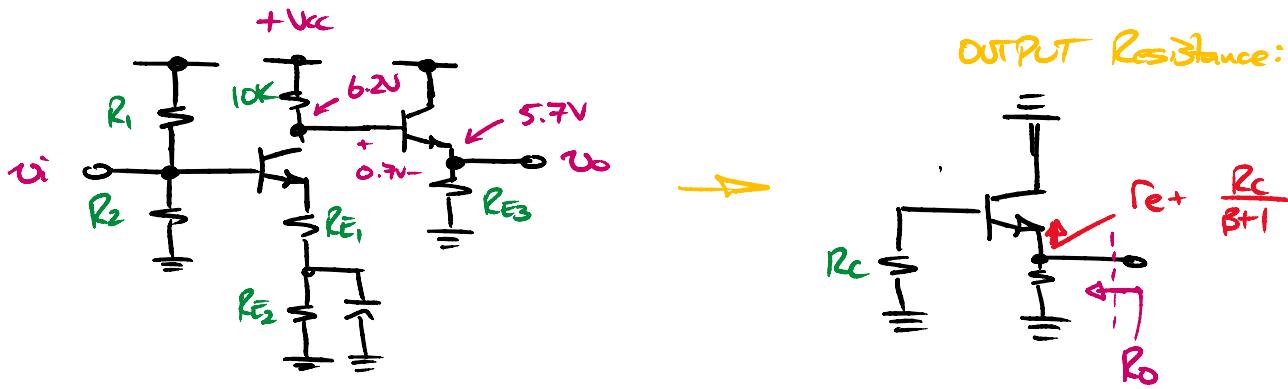→ We can solve the problem by adding a CC stage:



$$R_o = R_E \parallel \left[R_E + \frac{R_C}{B+1} \right]$$

to make sure that I_{B2} is 20 times smaller than I_{C1} . Could have made it 10 times too, just want significantly lower. Alternatively, you could use a DC-blocking cap at bias the second stage separately w/ another voltage divider.

$$\rightarrow R_E = \frac{5.5}{0.19} = 2.86k\Omega$$


$$\rightarrow I_{C2} = \beta I_{B2} = 1.9mA \rightarrow g_{m2} = 76mS$$

$$\rightarrow r_{e2} \approx \frac{1}{g_{m2}} = 0.013k\Omega$$

$$\rightarrow R_o = 2.86k\Omega \parallel \left[0.013 + \frac{10k}{10} \right] = 0.108k\Omega$$

0.112k\Omega

AMPLIFIER GAIN: - AC ANALYSIS

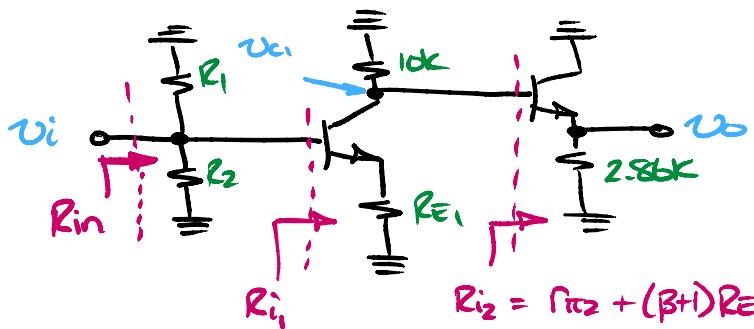

$$R_{i2} = R_{c2} + (\beta + 1)R_{E3}$$

$$= \frac{100}{76} + 101 \cdot 2.86$$

$$R_{i2} = 290.2\text{k} \text{ if } R_L = \infty$$

$$\rightarrow \frac{V_{C1}}{V_i} = \frac{-g_m(R_c/R_{i2})}{1 + g_m R_{E1}} = \frac{-15.2(10/290)}{1 + 15.2 \cdot 0.134} = -48.4\%$$

$$\rightarrow \frac{V_o}{V_{C1}} = \frac{g_m R_{E2}}{1 + g_m R_{E3}} = \frac{76 \cdot 2.86}{1 + 76 \cdot 2.86} = 0.995\%$$

$$\rightarrow A_{VO} = \frac{V_o}{V_i} \cdot \frac{V_{C1}}{V_i} = (48.4 \cdot 0.995) = -48.2\%$$

→ But we wanted a gain of 50, so let's increase it by adjusting R_{E1} :

Since we lost some gain to the CC: $\frac{V_{C1}}{V_i} = \frac{-50}{0.995} = -50.3\%$

↳ -50.3 is what we need
@ the CE to have a gain of 50 overall.

$$\rightarrow -50.3 = \frac{-15.2(10/290)}{1 + 15.2R_{E1}} \rightarrow R_{E1} = 0.126\text{k}\Omega$$

Meaning R_{E2} becomes: $R_{E2} = 5.47 - 0.126 \rightarrow R_{E2} = 5.34\text{k}\Omega$

The change in R_{E1} also changes the input resistance of the whole amp:

The change in β also changes the input resistance of the current amp:

$$R_{in} = r_{in} + (\beta+1)R_{E1} = \frac{100}{15.2} + 10 \cdot 0.126 \rightarrow R_{in} = 19.3\text{k}\Omega$$

To achieve $R_{in} = 10\text{k}\Omega$:

$$R_1 \parallel R_2 \parallel 19.3 = 10 \rightarrow R_1 \parallel R_2 = 20.8\text{k}\Omega$$

Since; $V_B = 2.8\text{V} \rightarrow 2.8 = 10 \cdot \frac{R_2}{R_1+R_2}$

Which results in $R_1 = 74.3\text{k}\Omega$ & $R_2 = 28.9\text{k}\Omega$

The current in the divider is: $I = \frac{10}{74.3 + 28.9}$

$$I = 0.099\text{mA} = 99\mu\text{A}$$

↳ which is $\ll 3.8\mu\text{A}$, so our assumption is valid.

FINAL AMPLIFIER DESIGN:

