

## Assignment problems: Chapter 1 and 2


### Chapter 1:

**1.3 (b & c):** Find the charge  $q(t)$  flowing through a device if the current is:

(b)  $i(t) = (2t + 5)\text{mA}, q(0) = 0$


(c)  $i(t) = 20\cos(10t + \pi/6)\mu\text{A}, q(0) = 2\mu\text{C}$

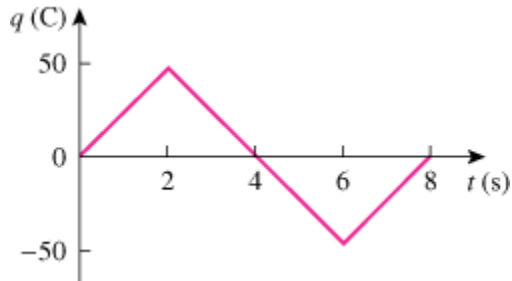**1.7:** The charge flowing in a wire is plotted in Fig below. Sketch the corresponding current.



**1.9:** The current through an element is shown in the Figure below. Determine the total charge that passed through the element at:

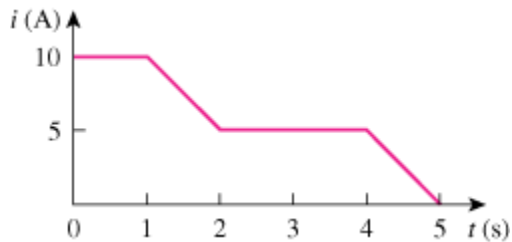
(a)  $t = 1\text{ s}$       (b)  $t = 3\text{ s}$       (c)  $t = 5\text{ s}$



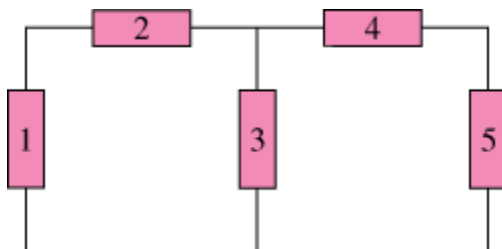
**1.17:** Figure below shows a circuit with five elements. If

$p_1 = -205\text{ W}, p_2 = 60\text{ W}, p_4 = 45\text{ W},$  and  $p_5 = 30\text{ W},$

calculate the power  $p_3$  absorbed by element 3.



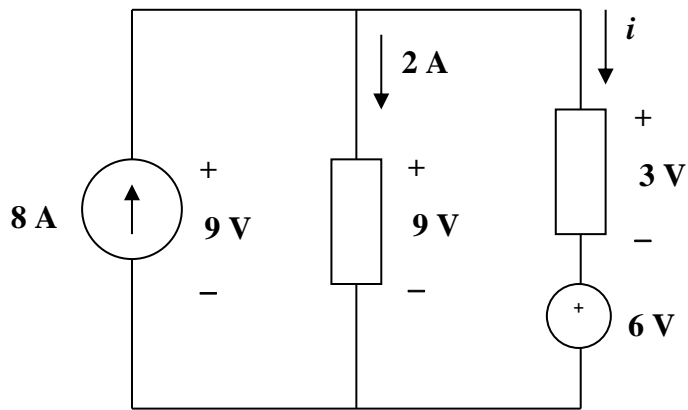
**1.19:** Find  $i$  in the network of Figure below:




**1.23:** A 1.8-kW electric heater takes 15 min to boil a quantity of water. If this is done once a day and power costs 10 cents per kWh, what is the cost of its operation for 30 days?

## Chapter 2:

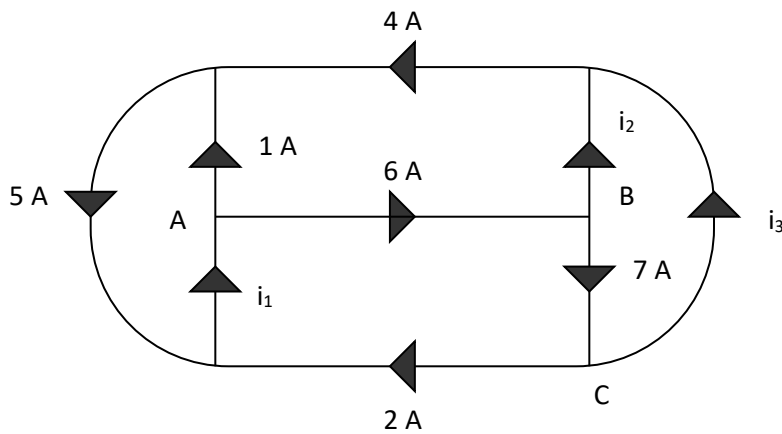
**2.9:** Find  $i_1$ ,  $i_2$ , and  $i_3$  in the following figure



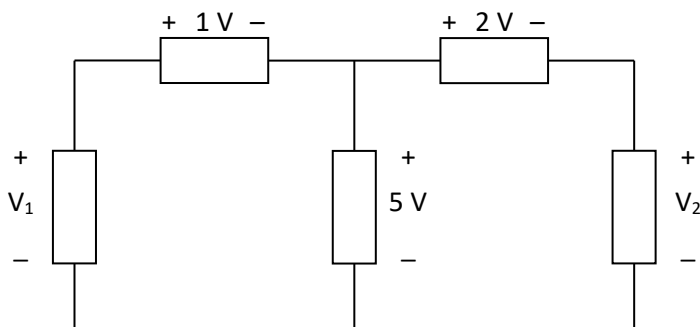
**2.11:** In the following circuit, calculate  $V_1$  and  $V_2$ .



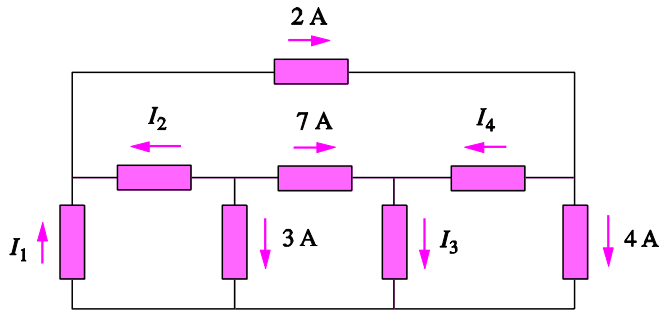
**2.13:** For the circuit in the following Figure, use KCL to find the branch currents  $I_1$  to  $I_4$ .



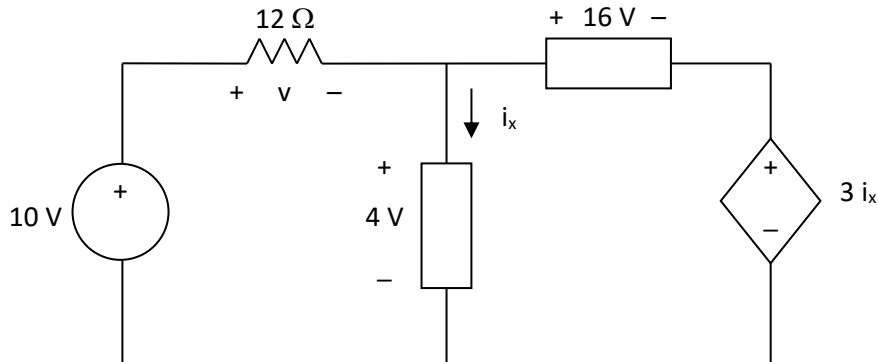
**2.15:** Calculate  $v$  and  $i_x$  in the following circuit.



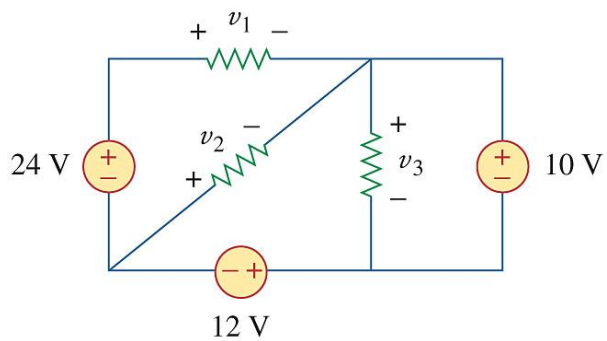
**2.17:** Obtain  $v_1$  through  $v_3$  in the following circuit.



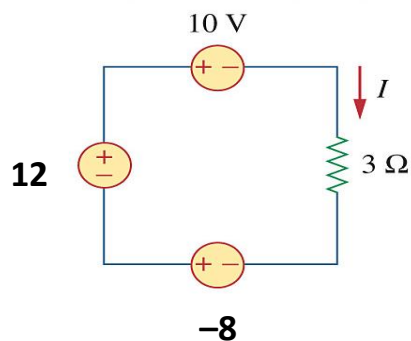
**2.19:** For the following circuit, find  $I$ , the power dissipated by the resistor, and the power supplied by each source.



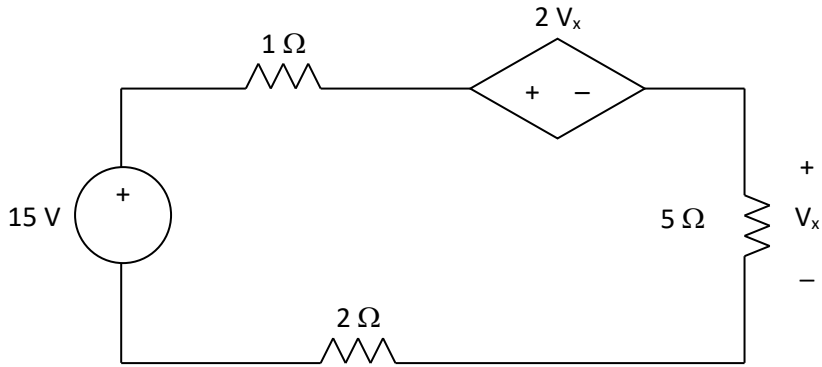
**2.21:** Find  $V_x$  in the following circuit.



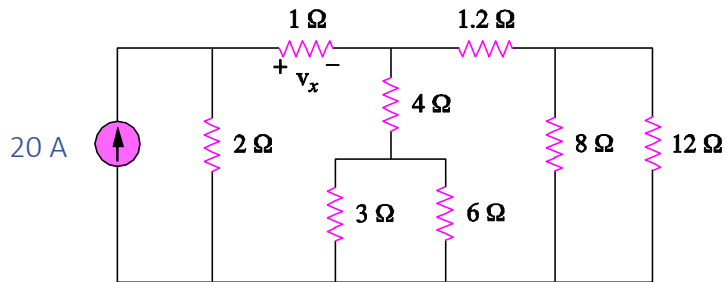
**2.23:** In the circuit shown below, determine  $v_x$  and the power absorbed by the  $12\text{-}\Omega$  resistor.



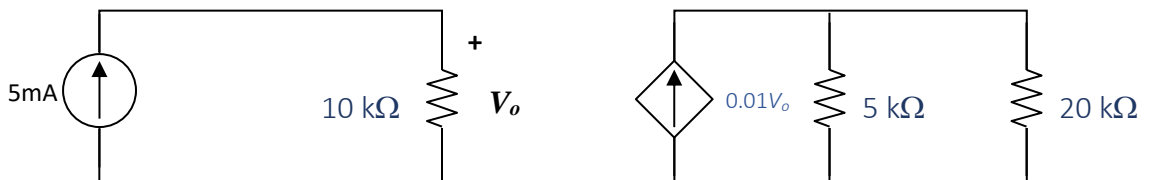
**2.25:** For the network shown below, find the current, voltage, and power associated with the 20-k $\Omega$  resistor.



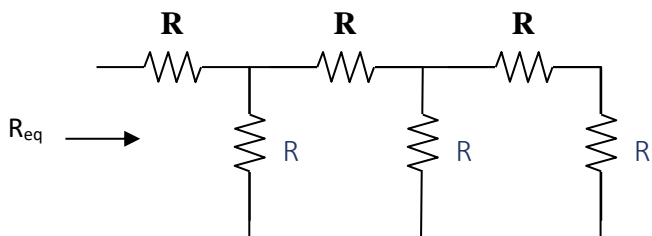
**2.29:** All resistors in the following circuit are  $5\ \Omega$  each. Find  $R_{eq}$ .



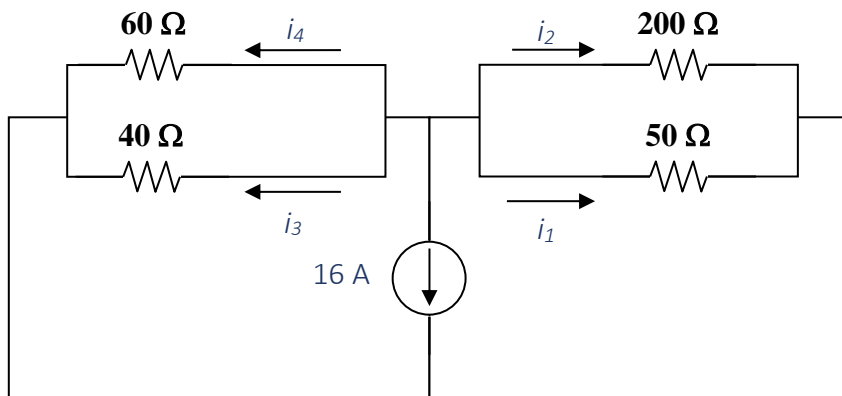
**2.32:** Find  $i_1$  through  $i_4$  in the following circuit.



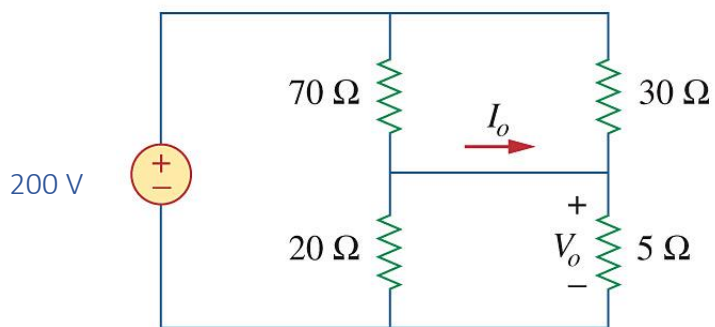
**2.35:** Calculate  $V_o$  and  $I_o$  in the following circuit.



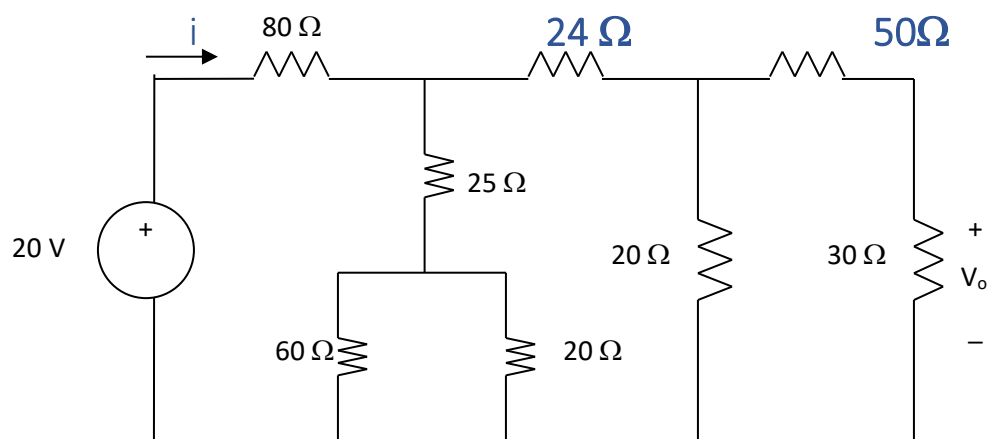
**2.36:** Find  $i$  and  $V_o$  in the following circuit.



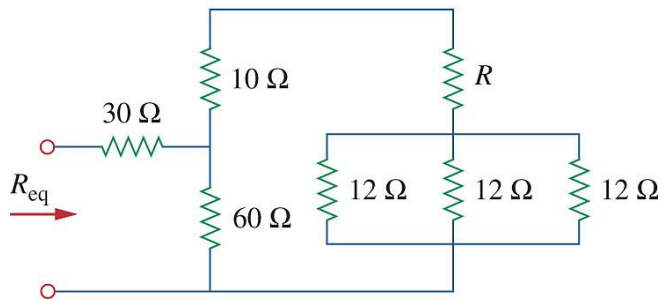**2.41:** If  $R_{eq} = 50\ \Omega$  in the following circuit, find  $R$ .



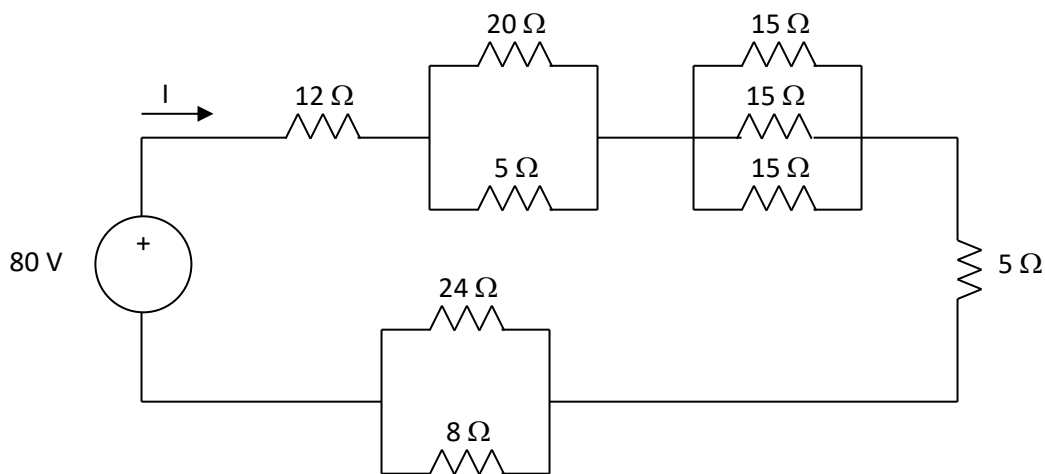**2.46:** Find  $I$  in the following circuit.



**2.47:** Find the equivalent resistance  $R_{ab}$  in the following circuit.

