

Analysis Vs synthesis

Analysis →
 → Straight-forward technique
 → Determine the function of an existing logic circuit

Synthesis →
 → Reverse technique
 → Design a circuit to implement a given function.

Goal: →
 → Simplify the function
 → Implement the function
 (minimum-cost logic circuit)

Tools: →
 → Truth Table
 → Timing diagram
 → Boolean algebra
 → Karnaugh map

Procedures: →
 → Determine sum-of-product function-
 (SOP)
 → or Determine product-of-sum
 (POS)
 → Design a canonical logic circuit
 → Simplify the SOP or POS function
 → Develop a minimum-cost circuit.

Functionally
equivalent circuit.

Boolean Algebra

(2)

Axioms

AND $\left\{ \begin{array}{l} 0 \cdot 0 = 0 \\ 0 \cdot 1 = 0 = 1 \cdot 0 \\ 1 \cdot 1 = 1 \end{array} \right.$

OR $\left\{ \begin{array}{l} 0 + 0 = 0 \\ 0 + 1 = 1 = 1 + 0 \\ 1 + 1 = 1 \end{array} \right.$

NOT $\left\{ \begin{array}{l} \bar{0} = 1 \\ \bar{1} = 0 \end{array} \right.$

Single variable

$$x \cdot 0 = 0$$

$$x \cdot 1 = x$$

$$x \cdot \bar{x} = 0$$

$$x \cdot x = x$$

$$x + 0 = x$$

$$x + 1 = 1$$

$$x + \bar{x} = 1$$

$$x + x = x$$

$$\bar{\bar{x}} = x$$

Two/Three variables

$$x \cdot y = y \cdot x$$

$$x + y = y + x$$

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

$$x + (y + z) = (x + y) + z$$

$$x + y \cdot z = (x + y)(x + z)$$

$$x + x \cdot y = x$$

$$x \cdot (1 + y) = x \cdot 1 = x$$

$$x \cdot y + x \cdot \bar{y} = x \cdot (y + \bar{y}) = x \cdot 1 = x$$

$$\begin{aligned} & (x + y) \cdot (x + \bar{y}) \\ &= \underline{x \cdot x} + x \cdot \bar{y} + x \cdot y + \underline{y \cdot \bar{y}} \\ &= x + x(\bar{y} + y) + 0 \\ &= x + x \cdot 1 = x + x = x \end{aligned}$$

$$\overline{x \cdot y} = \bar{x} + \bar{y}$$

$$\overline{x + y} = \bar{x} \cdot \bar{y}$$


De Morgan's theorem

$$\overline{x + y + z} = \bar{x} \cdot \bar{y} \cdot \bar{z}$$

$$\begin{aligned} \overline{x + y \cdot z} &= \bar{x} \cdot \overline{y \cdot z} \\ &= \bar{x} \cdot (\bar{y} + \bar{z}) \end{aligned}$$

Example-1 : Analysis

(3)

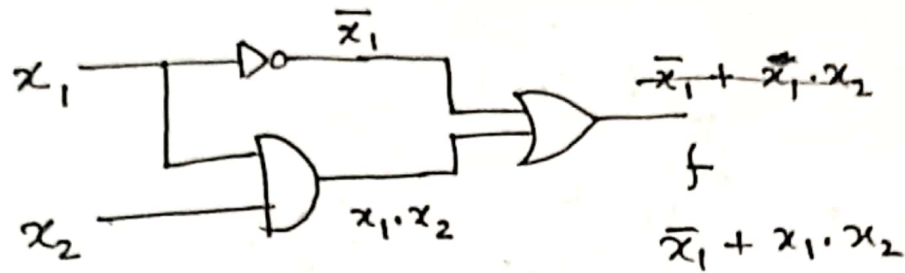


Given circuit

Function: $f(x_1, x_2) = \bar{x}_1 + x_1 \cdot x_2$

$f = \bar{x}_1 \cdot 1 + x_1 \cdot x_2$
 $= \bar{x}_1 \cdot (\bar{x}_2 + x_2) + x_1 \cdot x_2$ (How do we know to manipulate with this)
 $= \bar{x}_1 \cdot \bar{x}_2 + \bar{x}_1 \cdot x_2 + x_1 \cdot x_2$
 $= \bar{x}_1 \cdot \bar{x}_2 + \bar{x}_1 \cdot x_2 + \bar{x}_1 \cdot x_2 + x_1 \cdot x_2$ (How do we know to repeat this term)
 $= \bar{x}_1 (\bar{x}_2 + x_2) + x_2 (\bar{x}_1 + x_1)$
 $= \bar{x}_1 + x_2$ ← Simplified equation.

$x + \bar{x} = 1$

Simplification of the function

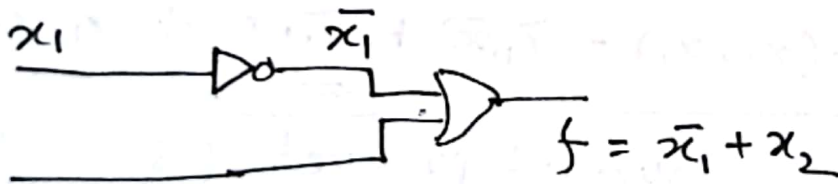

Simplified circuit

④

$$f = \bar{x}_1 + x_1 \cdot x_2$$

A B

Midterm
Oct 24

x_1	x_2	f
0	0	1
0	1	1
1	0	0
1	1	1

A	B
1	0
1	0
0	0
0	1

Forming
Truth Table from
a given function

Product terms \rightarrow minterms

x_1	x_2	Minterm
0 \leftarrow 0	0	1 $\bar{x}_1 \cdot \bar{x}_2$
1 \leftarrow 0	1	1 $\bar{x}_1 \cdot x_2$
2 \leftarrow 1	0	0 $x_1 \cdot \bar{x}_2$
3 \leftarrow 1	1	1 $x_1 \cdot x_2$

$$\bar{x}_1 \cdot \bar{x}_2$$


$$f(x_1, x_2) = \bar{x}_1 \cdot \bar{x}_2 + \bar{x}_1 \cdot x_2 + x_1 \cdot x_2$$

Sum of product (SOP) function

$$f(x_1, x_2) = \sum m(0, 1, 3)$$

Sop function

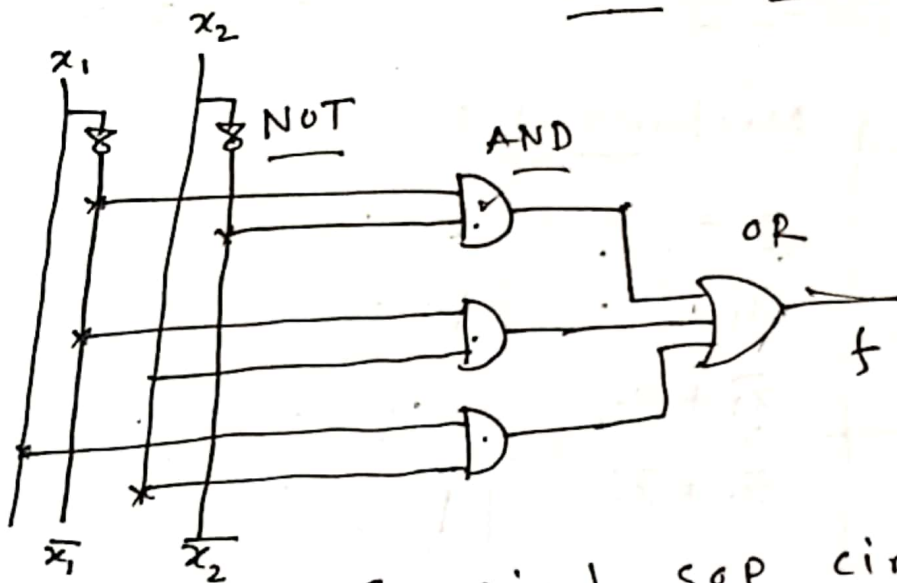
$$f(x_1, x_2) = \underline{\bar{x}_1 \bar{x}_2} + \underline{\bar{x}_1 x_2} + \underline{x_1 x_2}$$



Canonical sop circuit

Simplification
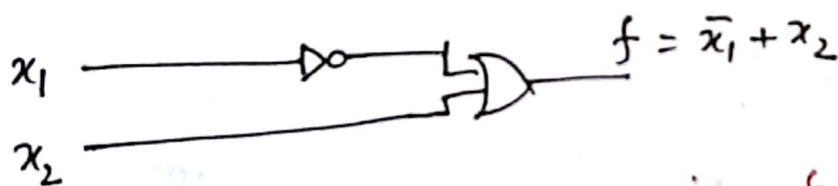
$$\begin{aligned} f &= \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + x_1 x_2 \\ &= \bar{x}_1 \bar{x}_2 + \bar{x}_1 x_2 + \bar{x}_1 x_2 + x_1 x_2 \\ &= \bar{x}_1 (\bar{x}_2 + x_2) + \cancel{\bar{x}_1} (\bar{x}_1 + x_1) x_2 \\ &= \underline{\bar{x}_1 + x_2} \end{aligned}$$



Simplified circuit from ^{the} SOP

POS : Product - of - sum
 AND OR

NOT - (OR) - AND

	x_1	x_2	Maxterms	f
0	0	0	$x_1 + x_2$	1 ✓
1	0	1	$x_1 + \bar{x}_2$	1 ✓
2	1	0	$\bar{x}_1 + x_2$	0 ✓
3	1	1	$\bar{x}_1 + \bar{x}_2$	1 ✓

POS Function: $f(x_1, x_2) = \prod M(2)$

$$f = \underline{\underline{\bar{x}_1 + x_2}}$$

Another Example



$f = (x_1 x_2) + (\bar{x}_1 x_2)$ → Given function

Truth Table

x_1	x_2	f
0	0	0
0	1	1
1	0	0
1	1	1

Sum $f = \sum m(1, 3)$

Pos $f = \prod M(0, 2)$

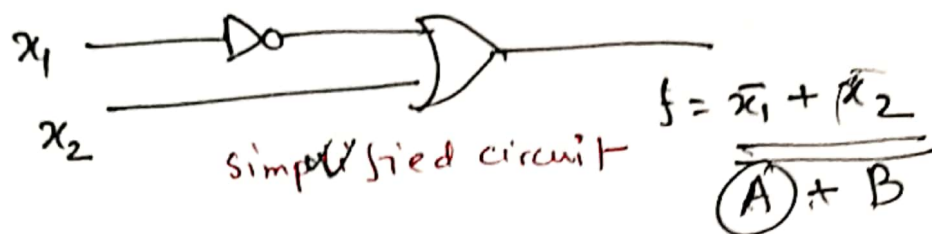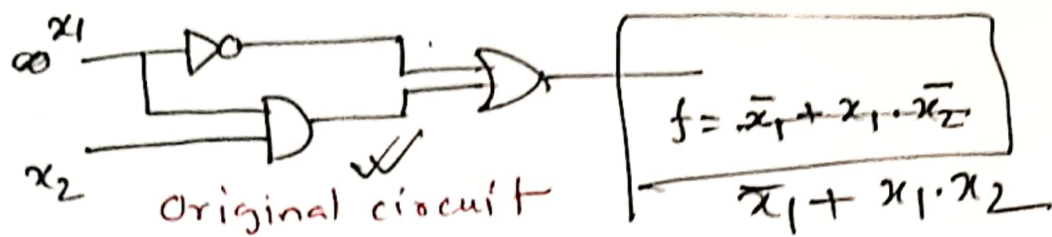

Truth Table of the original circuit (see page #4)

x_1	x_2	f
0	0	1
0	1	1
1	0	0
1	1	1

Truth Table of the simplified circuit

x_1	x_2	f
0	0	1
0	1	1
1	0	0
1	1	1

Functionally equivalent circuit

A	B
1	0
1	1
0	0
0	1

Timing diagram


③

Top
↓
bottom

Left to right →

x_1	x_2	f	A	B
0 ✓	0 ✓	1 ✓	1 ✓	0 ✓
0 ✓	1	1	1	0
1	0	0 ✓	0 ✓	0 ✓
1 ✓	1	1	0	1

Truth Table

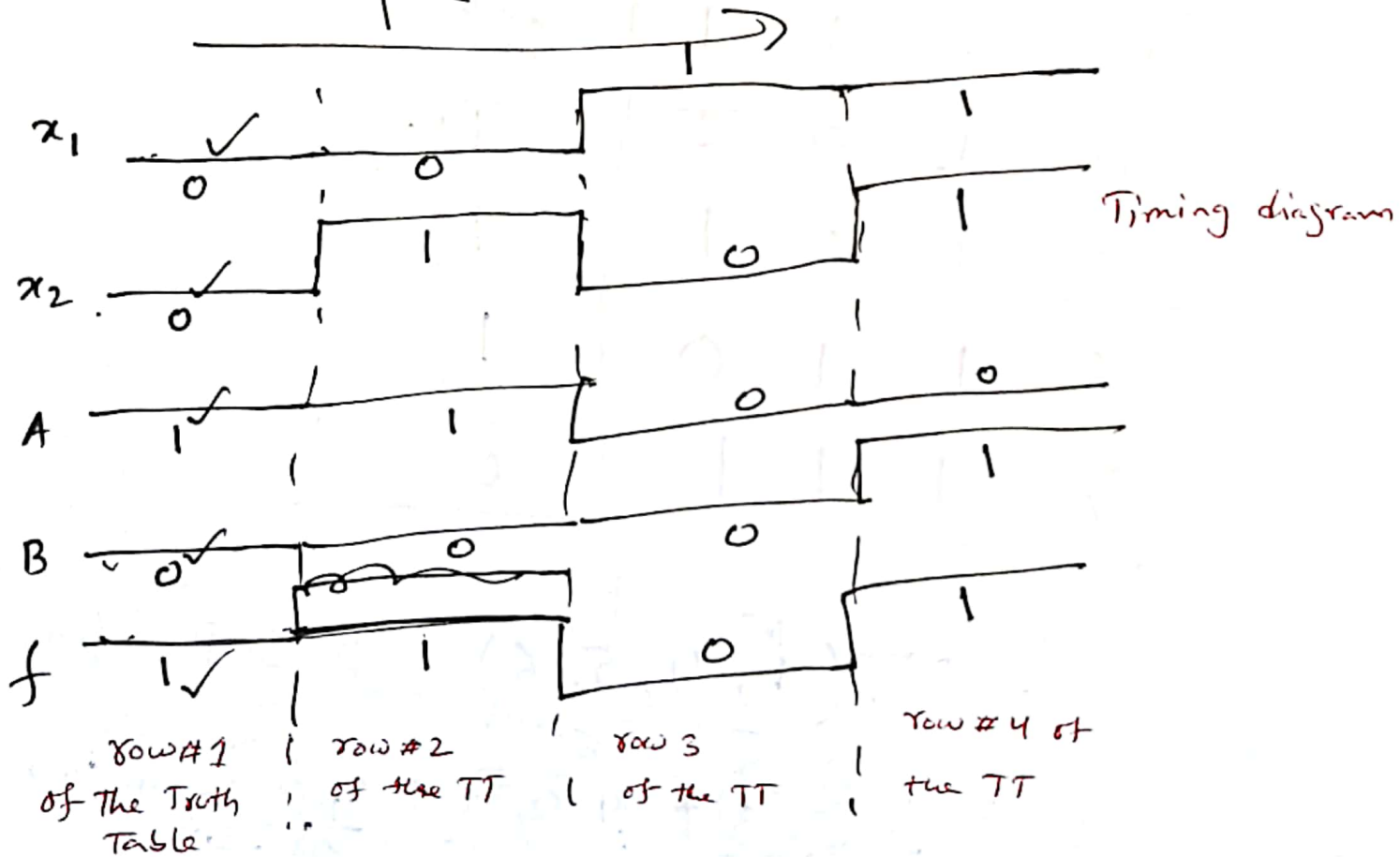

Another Example

A Given Truth Table

	x_1	x_2	x_3	f
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0 ✓
3	0	1	1	0 ✓
4 ✓	1	0	0	1 ✓
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

0	1	3	2
4	5	7	6

$$f = \Sigma(1, 4, 5, 6) \text{ SOP function}$$

$$= \bar{x}_1 \bar{x}_2 x_3 + x_1 \bar{x}_2 \bar{x}_3 + x_1 \bar{x}_2 x_3 + x_1 x_2 \bar{x}_3$$

$$= \bar{x}_2 x_3 (\bar{x}_1 + x_1) + x_1 \bar{x}_3 (\bar{x}_2 + x_2)$$

$$= \bar{x}_2 x_3 + x_1 \bar{x}_3 \quad \checkmark$$

Simplified equation

Draw the simplified circuit


POS

10

$$f = \prod (0, 2, \underline{3}, 7)$$

\bar{x}_1	x_1	\bar{x}_2	x_2
0	1	3	2
4	5	6	7

$$\begin{aligned}
 f &= (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3) \\
 &= \left[\underbrace{(x_1 + x_3) + \bar{x}_2}_{\substack{\text{X} \\ \bar{Y}}} \right] \cdot \left[\underbrace{(x_1 + x_3) + \bar{x}_2}_{\substack{\text{X} \\ \bar{Y}}} \right] \cdot \left[\underbrace{x_1 + (\bar{x}_2 + \bar{x}_3)}_{\substack{\text{X} \\ \bar{Y}}} \right] \cdot \left[\underbrace{\bar{x}_1 + (\bar{x}_2 + \bar{x}_3)}_{\substack{\text{X} \\ \bar{Y}}} \right] \\
 &= (x_1 + x_3)(\bar{x}_2 + \bar{x}_3)
 \end{aligned}$$

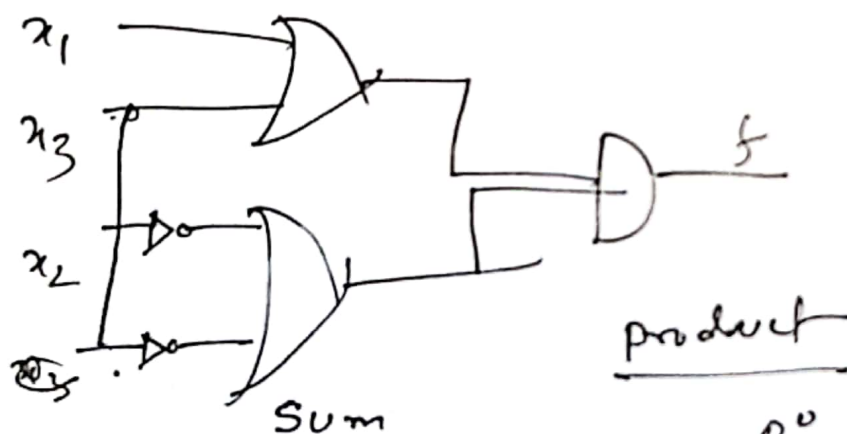

	$\bar{x}_1 \bar{x}_2$	$\bar{x}_1 x_2$	$x_1 \bar{x}_2$	$x_1 x_2$
\bar{x}_3	$\bar{x}_1 \bar{x}_2 \bar{x}_3$ (X)	$\bar{x}_1 x_2 \bar{x}_3$ (1)	$x_1 \bar{x}_2 \bar{x}_3$ (X)	$x_1 x_2 \bar{x}_3$ (X)
x_3	$\bar{x}_1 \bar{x}_2 x_3$ (4)	$\bar{x}_1 x_2 x_3$ (5)	$x_1 \bar{x}_2 x_3$ (X)	$x_1 x_2 x_3$ (7)