


COE328

Digital Electronics


Lecture 11

Dr. Shazzat Hossain

Multiplexer Application: Crossbar switch

 


 If $\underline{s=0}$ then $Y1=X2, Y2=X1$
If $\underline{s=1}$ then $Y1=X1, Y2=X2$



Multiplexer Extension

Implement a 4-to-1 MUX using 2-to-1 MUX

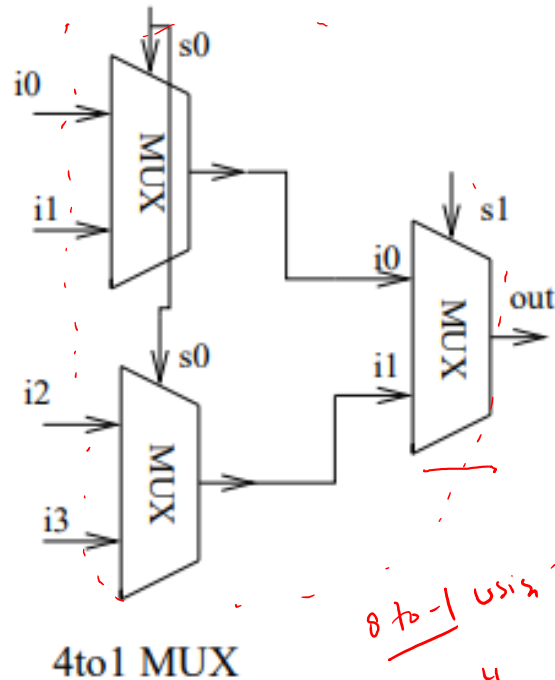

8 to 1 using 2 to 1
 1st $\frac{8}{2} = 4$
 2nd $\frac{4}{2} = 2$

No. of multiplexers

1st stage = $\frac{4}{2} = 2$

2nd stage = $\frac{2}{2} = 1$

16-to-1 using 2 to 1

1st stage = $\frac{16}{2} = 8$

2nd " = $\frac{8}{2} = 4$

8-to-1 4 to 1

1st $\frac{8}{4} = 2$

2nd $\frac{2}{4} = 0.5$


1st stage = $\frac{16}{4} = 4$

2nd stage = $\frac{4}{4} = 1$

3rd stage = $\frac{4}{2} = 2$

4th stage = $\frac{2}{2} = 1$

Implement a 16-to-1 MUX using 4-to-1 MUX

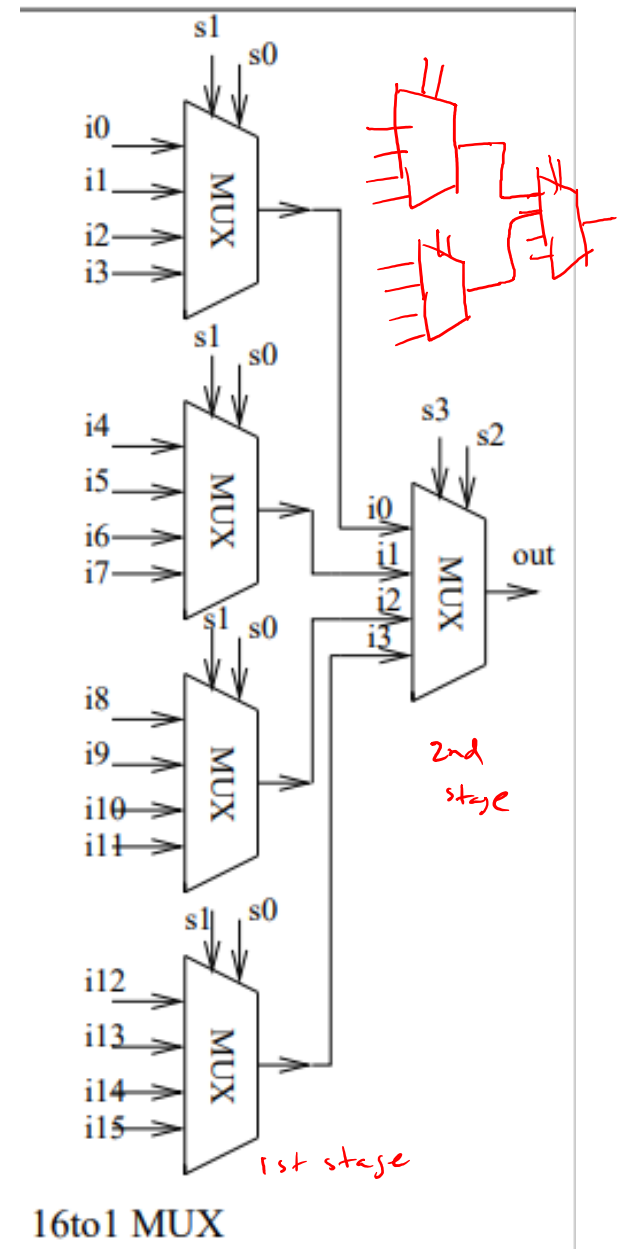

Function Implementation using LUT


Implement $f = \bar{w}_1 \bar{w}_3 + w_1 w_3 + w_1 w_2$

LUT for $g = \bar{w}_1 \bar{w}_3 + w_1 w_3$

w_1	w_3	$\bar{w}_1 \bar{w}_3 + w_1 w_3$
0	0	1
0	1	0
1	0	0
1	1	1

LUT for $k = w_1 w_2$

w_1	w_2	$w_1 w_2$
0	0	0
0	1	0
1	0	0
1	1	1

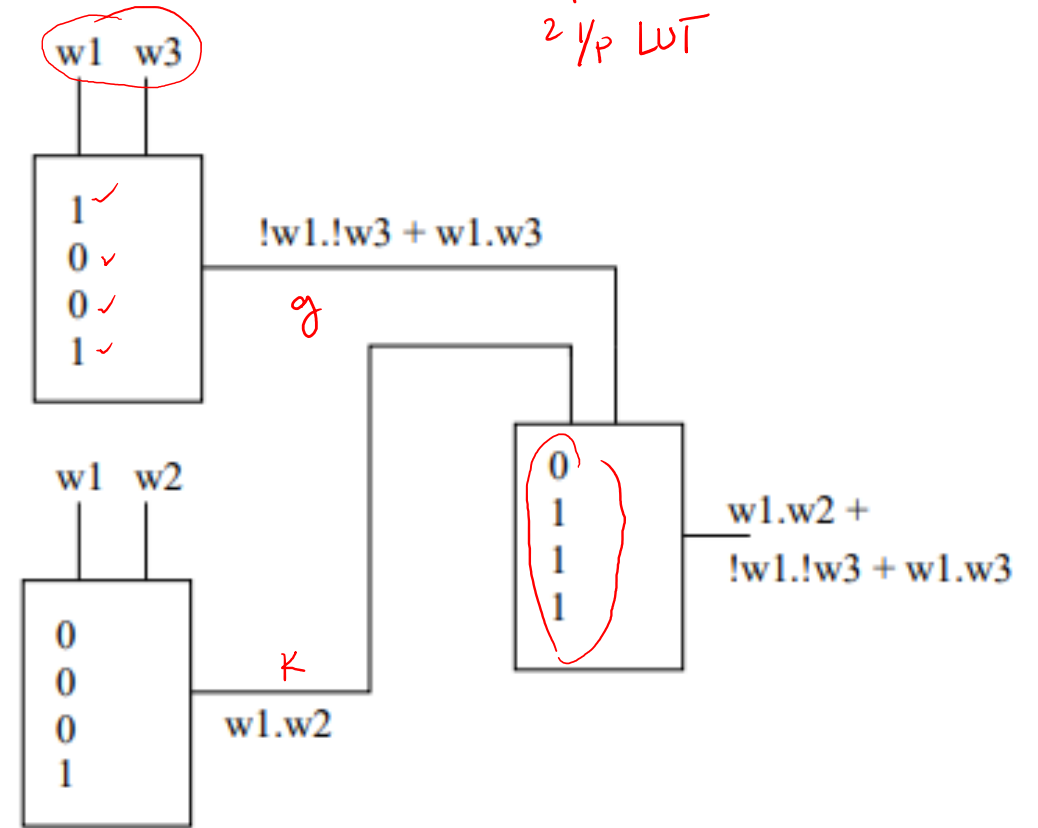

LUT for $f = g + k$

0
1
1
1

g	k	f
0	0	0
0	0	0
1	0	1
1	1	1


Demultiplexer

Multiple outputs from a single input, selected by select line(s).
Could use a decoder, with $E_n = \text{input}$.


DEMUX
 $n \rightarrow \text{select lines}$
 $2^n \rightarrow \text{I/P}$
 $1 \rightarrow \text{O/P} \rightarrow$

$n \leftarrow \text{select lines}$
 $1 \rightarrow \text{I/P}$
 $2^n \rightarrow \text{O/P}$

S_1	S_0	Output
0	0	y_0
0	1	y_1
1	0	y_2
1	1	y_3

 

DeMultiplexer

 

Encoder


From n inputs, one is active and the output is the code for the specific input.

Example: Binary encoder

Priority encoder:


w_3	w_2	w_1	w_0	y_1	y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Truth table

 

(b) Circuit

Figure 6.23 A 4-to-2 binary encoder.

 

Inputs				Outputs	
D_3	D_2	D_1	D_0	Q_1	Q_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1
0	0	0	0	X	X

Inputs				Output	
D_3	D_2	D_1	D_0	B	A
0	0	0	0	X	X
0	0	0	1	0	0
0	0	1	X	0	1
0	1	X	X	1	0
1	X	X	X	1	1

$$A = w_3 + \bar{w}_3 \bar{w}_2 w_1$$

$$B = w_3 + \bar{w}_3 w_2$$

Encoder

Hexadecimal to Binary encoder: Converts a hexadecimal number into a four-bit binary

 



Fig. 2-18 Hexadecimal encoder.

Application of Encoder

Encoder

Positional Encoders (Source: electronicshub.org)



A magnetic positional control is another common application of priority encoders. Such control is used in robotic arm positioning and ship navigations. In such cases, encoder converts the rotary or angular position of a compass to a digital code. Then this code is input to the computer so that the navigational data is provided. Below figure shows the simple compass encoder that converts the 8 positions to 3 bit output. For this type of input –output configuration, a 74LS148 IC is used which is an 8-to-3 line priority encoder. For indicating the compasses angular position, generally reed switches and magnets are used. application of priority encoder block diagram application of priority encoder

 

Compass Direction	Binary Output		
	Q ₀	Q ₁	Q ₂
North	0	0	0
North - East	0	0	1
East	0	1	0
South - East	0	1	1
South	1	0	0
South - West	1	0	1
West	1	1	0
North - West	1	1	1


Decoders → important

  N inputs generate 2^n outputs, with only one = true based on value of n.
For 2 inputs, we have 4 outputs.



Decoder Expansion

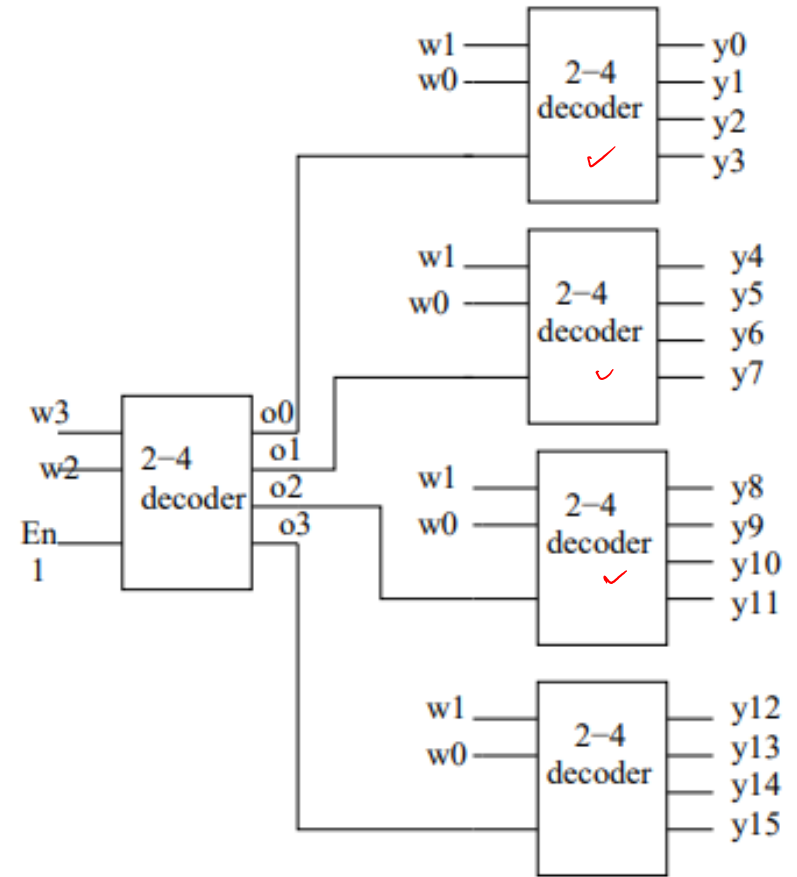Design a 16-output decoder using 4 output decoders



Decoder Expansion



CODE Conversion

From BCD to 7 segment display

Segment a = 0 + 2 + 3 + 5 + 6 + 7 + 8 + 9

Use a 4 to 16 decoder, then OR gate for each segment

w3	w2	w1	w0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	1	0	1	1

  

Code Converter

Arithmetic Comparator

5 ARITHMETIC COMPARISONS


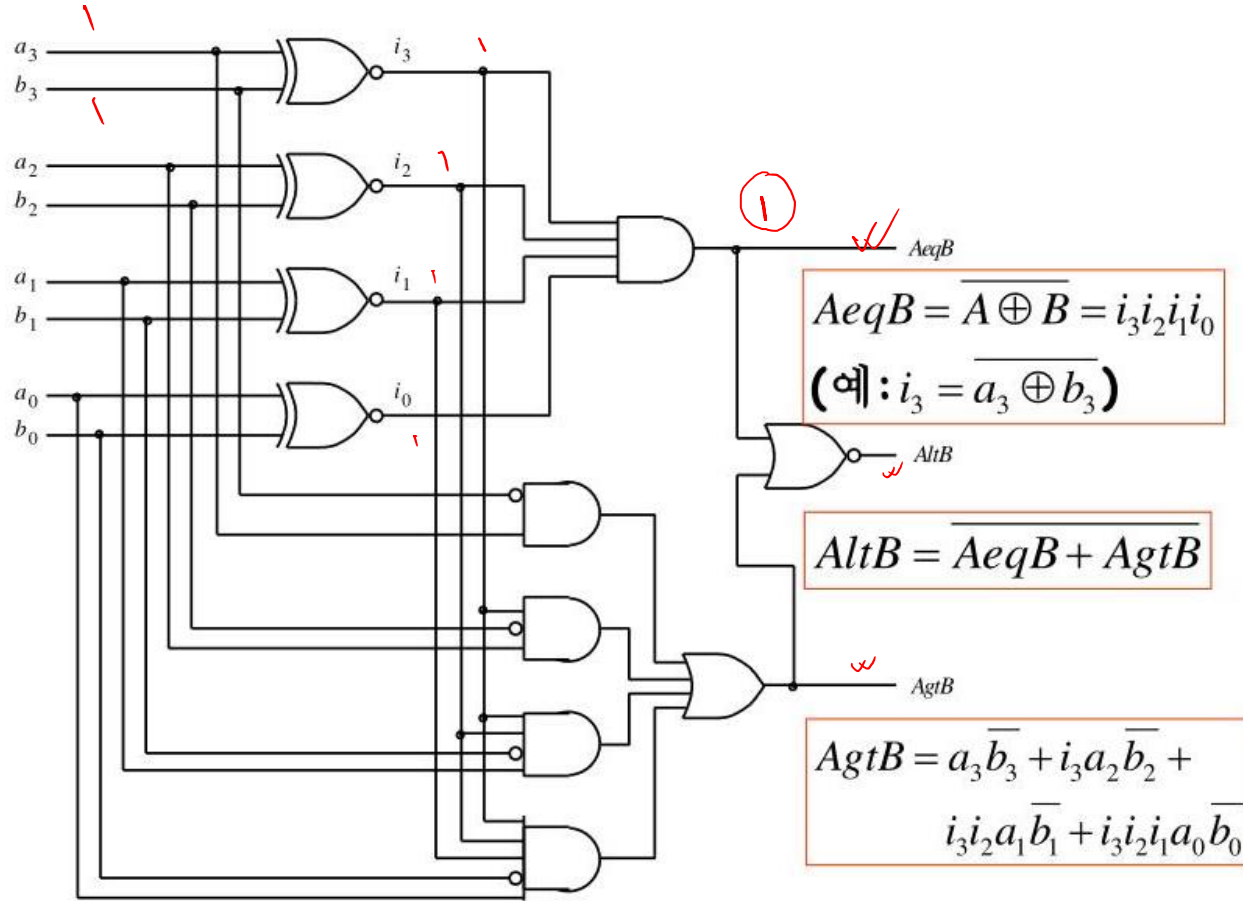


Figure 6.26. A four-bit comparator circuit.

 

VHDL Codes

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mux4to1 IS
    PORT( w0, w1, w2, w3: IN STD_LOGIC;
          s      : IN STD_LOGIC_VECTOR(1 DOWNT0 0);
          f      : OUT STD_LOGIC);
END mux4to1;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
    WITH s SELECT
        f<= w0 WHEN "00",
            w1 WHEN "01",
            w2 WHEN "10",
            w3 WHEN OTHERS;
END Behavior;
```

VHDL Codes

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dec2to4 IS
    PORT( w      : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          En     : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          y      : OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END dec2to4;

ARCHITECTURE Behavior OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR (2 DOWNTO 0);
BEGIN
    Enw <= En & w;
    WITH Enw SELECT
        y<= "1000" WHEN "100",
            "0100" WHEN "101",
            "0010" WHEN "110",
            "0001" WHEN "111"
            "0000" WHEN OTHERS;
END Behavior;
```

VHDL Code

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;


ENTITY encod IS
    PORT( w    : IN STD_LOGIC_VECTOR(3 DOWNT0 0);
          y    : OUT STD_LOGIC_VECTOR(1 DOWNT0 0);
          z    : OUT STD_LOGIC);
END encod;

ARCHITECTURE Behavior OF encod IS
BEGIN
    PROCESS(w)
    BEGIN
        IF w(3) = '1' THEN
            y <= "11";
        ELSEIF w(2) = '1' THEN
            y<= "10";
        ELSEIF w(1) = '1' THEN
            y<= "01";
        ELSE
            y<= "00";
        END IF;
    END PROCESS;
    z<= '0' WHEN w = "0000" ELSE "1";
END Behavior;
```

Example

 6.2. Use a 3-to-8 decoder and an OR gate to implement

$$f = \sum m(\underline{1, 2, 3, 5, 6})$$



$$\begin{aligned} g &= \bar{w}_3 + w_2\bar{w}_3 + w_2 \\ &= \bar{w}_2(\bar{w}_3) + w_2(1) \end{aligned}$$



$\begin{matrix} 1+x+x \\ =1 \end{matrix}$

6.3. Use 2-to-1 MUX to implement $f = \bar{w}_1\bar{w}_3 + w_2\bar{w}_3 + \bar{w}_1w_2$

only

has no w_1
  
$$\begin{aligned} f &= \bar{w}_1(\bar{w}_3 + w_2\bar{w}_3 + w_2) + w_1(w_2\bar{w}_3) \\ &= \bar{w}_1g + w_1h \end{aligned}$$



$$\begin{aligned} h &= w_2\bar{w}_3 \\ &= \bar{w}_2(0) + w_2(\bar{w}_3) \end{aligned}$$

$$\begin{aligned} k &= \bar{w}_3 \\ &= \bar{w}_3(1) + w_3(0) \end{aligned}$$