

# VHDL for Sequential Circuits

COE 328-022 Pei Yang


Nov 14 2022

## Introduction:

The objective of this lab was to explore Moore and Mealy machines by designing and simulating an FSM to cycle through our student IDs.

## Pre Lab:

The machine given was a mealy FSM # 2.

 


State/State Assigned table:

present state	next state		Output	
	w=0	w=1	w=0	w=1
S <sub>0</sub>	S <sub>0</sub>	S <sub>1</sub>	d <sub>1</sub>	d <sub>2</sub>
S <sub>1</sub>	S <sub>1</sub>	S <sub>3</sub>	d <sub>2</sub>	d <sub>3</sub>
S <sub>2</sub>	S <sub>2</sub>	S <sub>0</sub>	d <sub>9</sub>	d <sub>1</sub>
S <sub>3</sub>	S <sub>3</sub>	S <sub>5</sub>	d <sub>3</sub>	d <sub>4</sub>
S <sub>4</sub>	S <sub>4</sub>	S <sub>2</sub>	d <sub>8</sub>	d <sub>7</sub>
S <sub>5</sub>	S <sub>5</sub>	S <sub>7</sub>	d <sub>4</sub>	d <sub>5</sub>
S <sub>6</sub>	S <sub>6</sub>	S <sub>4</sub>	d <sub>7</sub>	d <sub>8</sub>
S <sub>7</sub>	S <sub>7</sub>	S <sub>8</sub>	d <sub>5</sub>	d <sub>6</sub>
S <sub>8</sub>	S <sub>8</sub>	S <sub>6</sub>	d <sub>6</sub>	d <sub>0</sub>


present state	next state				output			
	y <sub>3</sub>	y <sub>2</sub>	y <sub>1</sub>	y <sub>0</sub>	w=0	w=1	w=0	w=1
S <sub>0</sub>	0	0	0	0	0000	0001	d <sub>1</sub>	d <sub>2</sub>
S <sub>1</sub>	0	0	0	1	0001	0011	d <sub>2</sub>	d <sub>3</sub>
S <sub>2</sub>	0	0	1	1	0011	0101	d <sub>9</sub>	d <sub>1</sub>
S <sub>3</sub>	0	1	0	1	0101	0111	d <sub>3</sub>	d <sub>4</sub>
S <sub>4</sub>	0	1	1	1	0111	1000	d <sub>8</sub>	d <sub>7</sub>
S <sub>5</sub>	1	0	0	0	1000	0110	d <sub>4</sub>	d <sub>5</sub>
S <sub>6</sub>	0	1	1	0	0110	0100	d <sub>7</sub>	d <sub>8</sub>
S <sub>7</sub>	0	1	0	0	0100	0010	d <sub>5</sub>	d <sub>6</sub>
S <sub>8</sub>	0	0	1	0	0010	0000	d <sub>6</sub>	d <sub>0</sub>

## Logic Equations:


w = 1

 

 
$$y_0 = y_3 y_2 y_1 + y_3 y_2 + y_3 y_1 y_0$$


 
$$y_1 = y_3 y_2 y_0 + y_3 y_2 y_1 + y_3 y_1 y_0$$



 
$$y_2 = y_3 y_2 y_1 y_0 + y_3 y_2 y_1 y_0 + y_3 y_2 y_1 y_0 + y_3 y_2 y_1 y_0$$




$$y_3 = y_3 y_2 y_1 y_0$$


w = 0

 


$$y_0 = y_3 y_1 y_0 + y_3 y_1 y_0$$

 

$$y_1 = y_3 y_1$$

 


$$y_2 = y_3 y_2$$

 


$$y_3 = y_3 y_2 y_1 y_0$$

## Logic Diagram:

 
 
## Experiment:

According to the FSM, the states and their outputs should follow the diagram below.



A skeleton code for the machine was provided in the lab manual. However, the state linking and state assignments would be written depending on our student numbers, FSM machine assigned, and choice of Mealy/Moore. In this lab, the machine used was a #2 FSM Mealy Machine. The code and waveform have been posted below.

The final waveform displays my student number and states in their order. The student number is displayed in 8 bit form using the sseg block, which accepts 4 bit binary input from the FSM and converts the given into the 8 bit output. The due to the way the sseg VHDL was written, the output given by Leds is missing its rightmost value, which is the value of Leds[7]. Since the state waveforms are also the 8 bit output of a sseg block, the waveform generated also needs to be interpreted this way (under the group name Ledss).

In the VHDL, the first process will move from the current state to the next one assigned when the clock is high, otherwise the state will stay the same when clock is low. The second process will assign a 4 bit binary number to the variables `current_state` and `student_id` which will eventually be fed to the ssegs.

## Conclusion:

There were some issues relating to incorrect values displaying in the waveform, however that was due to accidentally writing the incorrect values in the second process of the FSM block.

```

library ieee;
use ieee.std_logic_1164.all;

entity lab5 is
port(clk,data_in,reset:in std_logic;
      student_id,current_state:out std_logic_vector(3 downto 0));
end lab5;

architecture fsm of lab5 is
type state_type is (s0,s1,s2,s3,s4,s5,s6,s7,s8);
signal yfsm:state_type;
begin
process(clk,reset)
begin
    if reset = '1' then
        yfsm<=s0;
    elsif(clk'event and clk='1')then

        case yfsm is
        when s0 => if data_in = '1' then yfsm <=s1;
                    else yfsm<=s0;end if;
        when s1 => if data_in = '1' then yfsm <=s3;
                    else yfsm<=s1;end if;
        when s2 => if data_in = '1' then yfsm <=s0;
                    else yfsm<=s2;end if;
        when s3 => if data_in = '1' then yfsm <=s5;
                    else yfsm<=s3;end if;
        when s4 => if data_in = '1' then yfsm <=s2;
                    else yfsm<=s4;end if;
        when s5 => if data_in = '1' then yfsm <=s7;
                    else yfsm<=s5;end if;
        when s6 => if data_in = '1' then yfsm <=s4;
                    else yfsm<=s6;end if;
        when s7 => if data_in = '1' then yfsm <=s8;
                    else yfsm<=s7;end if;
        when s8 => if data_in = '1' then yfsm <=s6;
                    else yfsm<=s8;end if;
        end case;
    end if;
end process;

process (yfsm,data_in)
begin
    case yfsm is
    when s0 =>current_state <="0000";
                if data_in='1' then student_id<="0101";
                    else student_id<="0000";
                end if;
    when s1=>current_state<="0001";
                if data_in='1' then student_id<="0000";
                    else student_id<="0001";
                end if;
    when s2=>current_state<="0010";
                if data_in='1' then student_id<="1001";
                    else student_id<="0010";
                end if;
    when s3=>current_state<="0011";
                if data_in='1' then student_id<="0001";
                    else student_id<="0011";
                end if;
    when s4=>current_state<="0100";

```



```

        if data_in='1' then student_id<="0101";
        else student_id<="0100";
        end if;
    when s5=>current_state<="0101";
        if data_in='1' then student_id<="0001";
        else student_id<="0101";
        end if;
    when s6=>current_state<="0110";
        if data_in='1' then student_id<="0110";
        else student_id<="0110";
        end if;
    when s7=>current_state<="0111";
        if data_in='1' then student_id<="0011";
        else student_id<="0111";
        end if;
    when s8=>current_state<="1000";
        if data_in='1' then student_id<="0111";
        else student_id<="1000";
        end if;
    when others =>current_state <="1111";
    Student_id <="1111";

end case;
end process;

end fsm;

```

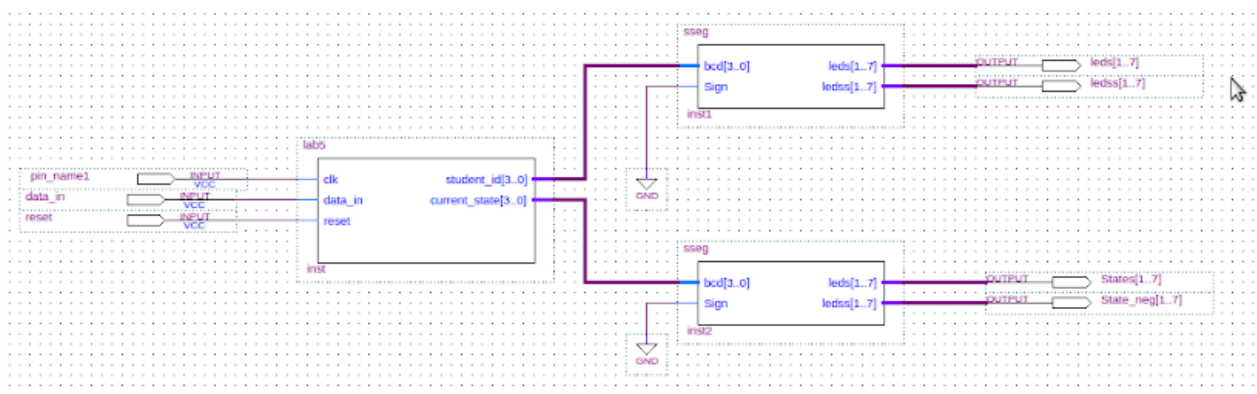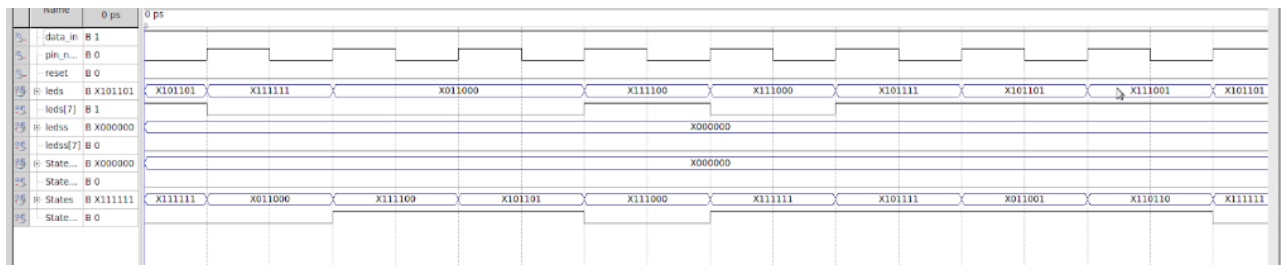

Conclusion:

