

ELE 302 Laboratory #5

Mutual Inductance

1.0 INTRODUCTION:

When a time-varying current flows in a coil, it generates a time-varying magnetic flux in the space surrounding it. The time-varying magnetic flux induces a voltage in any conductor linked by this flux. Thus, if a second coil exists in a close physical proximity, an induced voltage will be generated across its terminals; its value is related to the time-varying current in the first coil by a parameter known as mutual inductance. Although the coils are physically separate, their interaction is due to the magnetic coupling that exists between them. The practical application of magnetic-coupling is important, especially in electrical power systems and communication systems.

2.0 OBJECTIVES:

- To determine the dot-convention of a given magnetically-coupled set.
- To measure the resistive and inductive parameters of the set.
- To verify the measured-value of the mutual inductance of the set by using an alternative method: measurement of mutual inductance as a function of self-inductance.
- To examine the concept of impedance reflection between magnetically-coupled networks.

3.0 REQUIRED LAB EQUIPMENT & PARTS:

- Function Generator (FG) and Oscilloscope.
- ELE202 Lab Kit and ELE302 Lab Kit: various components, breadboard, wires and jumpers.
- Magnetically-Coupled Coils (from your TA).

4.0 PRE-LAB ASSIGNMENT (3 marks with 1.5 marks for each step):

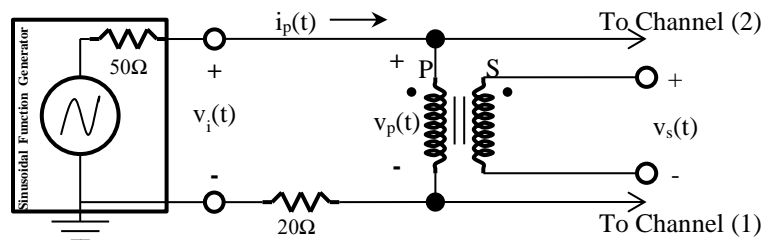



Figure 1.0: Measuring Parameters of Magnetically-Coupled Coils

- (a) Step 1: The circuit shown in **Figure 1.0** consists of magnetically-coupled coils, where the primary coil is connected in series with a sinusoidal source and a current-sampling 20Ω -resistor, while the secondary coil is open-circuit; i.e., has no load (NL).

The primary coil has self-inductance L_p and inherent resistance R_p , and the secondary coil has self-inductance L_s and inherent resistance R_s ; the mutual inductance between the two coils is M .

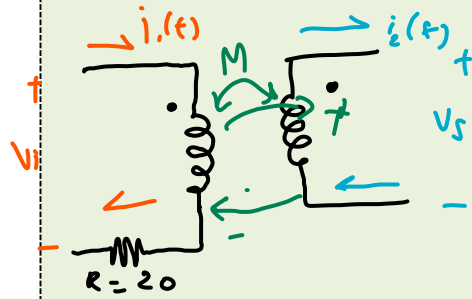- i) Determine the expressions for V_i and V_s in terms of I_p and the coils parameters, where V_i , V_s and I_p are the phasors for $v_i(t)$, $v_s(t)$ and $i_p(t)$, respectively.

Pre-Lab workspace (show your analysis here)



$$-V_i + R i + j\omega L i = 0$$

$$-V_i + R i + j(-j\omega L) = 0$$

$$V_i = j\omega L i - R i$$


$$V_i = i(j\omega L - R)$$

$$V_s - j\omega M i = 0$$

$$V_s = j\omega M i$$

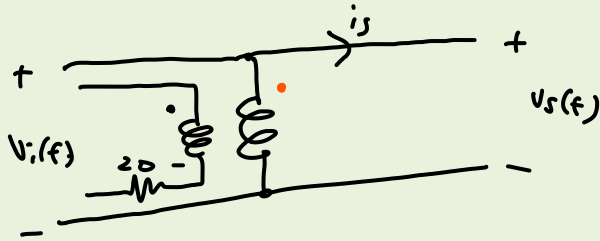- ii) Suppose that the primary and secondary coils are interchanged; i.e., the primary terminals are now open circuited, and the current flow through L_s is $i_s(t)$. Find the expressions for V_i and V_p in terms of I_s and the coils parameters, where V_i , V_s and I_s are the phasors for $v_i(t)$, $v_s(t)$ and $i_s(t)$, respectively.

Pre-Lab workspace (show your analysis here)



$$V_i = j\omega M i$$

$$V_s = R_s i + 20 i + j\omega M i$$

$$= (R_s + 20 + j\omega M) i$$

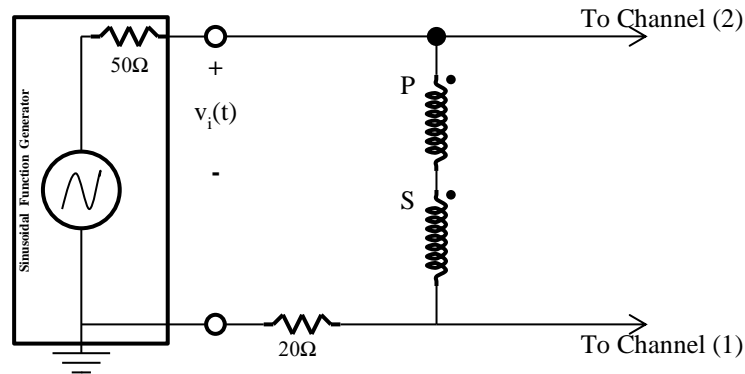


Figure 2.0: Measuring Mutual Inductance as Self-Inductance

- (b) Step 2: The primary and secondary coils shown in **Figure 2.0** are connected in series-aiding with the current $i(t)$ entering each of the coils from its dotted terminal. Let the total inductance of this arrangement be L_A . Upon interchanging the secondary terminals connections, however, total inductance of the series-opposing arrangement becomes L_B .

Show that the mutual inductance M is:

$$M = \frac{L_A - L_B}{4}$$

Pre-Lab workspace (show your analysis here)

L_A :

$$V_1 = L_T \frac{di}{dt}$$

$$= (L_1 + L_2 + 2M) \frac{di}{dt}$$

$$V_1 = L_A \frac{di}{dt}$$

L_B :

$$V_2 = L_T \frac{di}{dt}$$

$$= (L_1 + L_2 - 2M) \frac{di}{dt}$$

$$V_2 = L_B \frac{di}{dt}$$

$$L_A - L_B = (L_1 + L_2 + 2M) - (L_1 + L_2 - 2M)$$

$$= \cancel{L_1} - \cancel{L_1} + \cancel{L_2} - \cancel{L_2} + 2M + 2M$$

$$L_A - L_B = 4M$$

$$M = \frac{L_A - L_B}{4}$$

5.0 IN-LAB IMPEMENTATION & MEASUREMENTS (5 marks in total):

Part I: Measurements of the Parameters of the Magnetically-Coupled Coils

- (a) Step 1: Connect the circuit shown in **Figure 1.0**. Connect Channel (1) of the oscilloscope to display the voltage across the 20Ω -current-sampling resistor (please use the 20Ω -resistor from the green-resistance box), and Channel (2) to display the voltage $v_i(t)$. By setting the trigger source at Channel (1) on the *falling edge*, the input current is now selected as the reference sinusoid.

Set the function generator to provide a sinusoidal input voltage $v_i(t)$ of maximum value at a frequency of 50kHz. [$v_i(t)$ maximum should be approximately 0.6V]

- (b) Step 2: Use the oscilloscope to measure the phase angle ϕ of $v_i(t)$ relative to $i_p(t)$, and the peak values of $v_i(t)$ and $v_{20\Omega}(t)$. *Note that, after pushing the "Auto Scale" button, you might have to adjust the horizontal time scale knob and the trigger knob to get a stable read out on the oscilloscope.*

Determine the no-load input impedance $Z_{i(NL)}$ seen by the source, as:

$$Z_{i(NL)} = \frac{V_i}{I_p} = 20 + R_p + jX_p$$

Find the numerical values of X_p ($\omega L_p = 2\pi f L_p$) and R_p . Record your results in **Table 1.0**.

Table 1.0 (0.5 marks)

ϕ (degree)	$ V_i $ (mV)	$ I_p $ (mA)	$Z_{i(NL)}$ (Ω)	X_p (Ω)	R_p (Ω)
72.57	311.13	12.73	24.4273	23.28	7.31

- (c) Step 3: Use Channel (2) to display the open-circuit voltage $v_s(t)$, and measure the phase-angle of $v_s(t)$ relative to $i_p(t)$.

Suppose that the top terminal of the primary coil in **Figure 1.0** is selected as the dotted terminal, then based on your phase measurement, which terminal of the secondary coil should be dotted?
.....

Measure the peak value of $v_s(t)$. Find the numerical value of the mutual inductance M , and record your results in **Table 2.0**.

Table 2.0 (0.5 marks)

$ V_s $ (mV)	$\angle V_s \text{ to } i$ (degrees)	X_M (Ω)
141.42	90.0	18.38

- (d) Step 4: Interchange the primary and secondary coils; the primary terminals are now open circuited, and the reference phasor is I_s , instead of I_p . Repeat your measurements as in Step 2 and Step 3. Evaluate the numerical values of X_s , R_s , and X_M ($\omega M = 2\pi f M$), and record your results in **Table 1.0** and **Table 2.0**.

Table 3.0 (0.5 marks)

ϕ (degree)	$ V_i $ (mV)	$ I_s $ (mA)	$Z_{i(NL)}$ (Ω)	X_s (Ω)	R_s (Ω)
41.1	393.98	16.97	23.33	15.34	17.6

Table 4.0 (0.5 marks)

$ V_p $ (mV)	$\angle V_p \text{ to } i$ (degrees)	X_M (Ω)
509.12	90.0	25.45

- (e) Step 5: Draw the equivalent circuit of the magnetically-couple coils in the time domain indicating the values of its parameters. Use a numerical value for M that is equal to the average value for M found from Table 2.0 and Table 4.0.

Find the value of the coefficient of coupling:

$$k = \frac{M}{\sqrt{L_p L_s}} = \frac{X_M}{\sqrt{X_p X_s}}$$


$$k = \frac{X_M}{\sqrt{X_p X_s}}$$

$$= \frac{(18.38 + 25.45)}{2}$$

$$\frac{\sqrt{(23.28)(15.39)}}{21.915}$$

$$= \frac{18.8975}{21.915}$$

$$k = 1.16$$

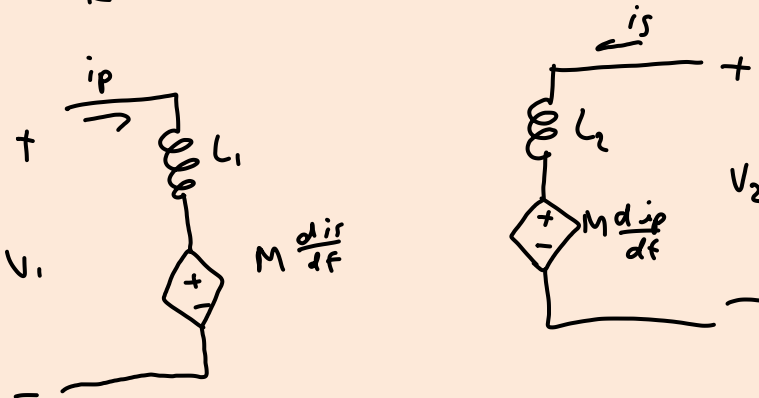

- (f) Step 6: Demonstrate Step 1 to Step 5 to your TA. (1 mark)

Part II: Measurement of the Mutual Inductance as a Self-Inductance

- (g) Step 7: Modify your circuit connections as shown in **Figure 2.0**, where the coils are connected in series-aiding arrangement. Repeat your measurements as in Step 2, and determine the value of X_A . Record your results in **Table 5.0**. Note that angle ϕ in this case is the phase angle of $v_i(t)$ relative to $i(t)$.

Table 5.0 (0.5 marks)

ϕ (degree)	$ V_i $ (mV)	$ I $ (mA)	$Z_i = V_i / I$ (Ω)	X_A (Ω)
83	388.9	2.3	169.1	167.8

- (h) Step 8: Interchange the connections of the secondary terminals; the coils are now in series-opposing form. Repeat your measurements as in Step 2, and determine the value of X_B . Record your results in **Table 6.0**:

Table 6.0 (0.5 marks)

ϕ (degree)	$ V_i $ (mV)	$ I $ (mA)	$Z_i = V_i / I$ (Ω)	X_B (Ω)
47	439.9	12.8	33.8	24.7

Determine the value of X_M as:

$$X_M = \frac{X_A - X_B}{4} = \frac{167.8 - 24.7}{4} = 35.78$$

- (i) Step 9: Demonstrate Step 7 and Step 8 to your TA. (1 mark)

6.0 POST-LAB QUESTIONS (2 marks in total, 1 mark for each question):

- (1) In comparing the different methods of measuring the value of the mutual inductance between the two coils, which one would you consider to be more reliable? Explain your answer.


- Inductors connected in series produces a more accurate M , since M is not solely reliant on mag field, which can be influenced by ext forces.

- (2) Suppose the coefficient of coupling between the two coils is close to unity, what would be the value of the turn ratio of the coils set? k

$$k = \frac{M}{\sqrt{L_1 L_2}}$$

$$\frac{N_2}{N_1} = ?$$

$$M = k \sqrt{L_1 L_2}$$

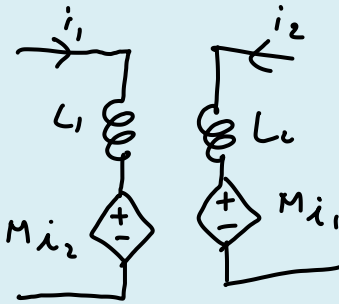

$$L = N \phi$$

$$N_1 \phi = L_1 i_1 + M i_2$$

$$N_2 \phi = L_2 i_2 + M i_1$$

$$N_1 \phi = L_1 i_1 + k i_2 \sqrt{L_1 L_2}$$

$$N_2 \phi = L_2 i_2 + k \sqrt{L_1 L_2} i_1$$

$$\frac{N_2}{N_1} = \frac{\sqrt{L_1}}{\sqrt{L_2}}$$

$$\frac{N_2}{N_1} = \sqrt{\frac{L_1}{L_2}}$$