



# Multiplexer

①

	s	x <sub>1</sub>	x <sub>2</sub>	f
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	1

$$\text{SOP } f = \sum m(2, 3, 5, 7)$$

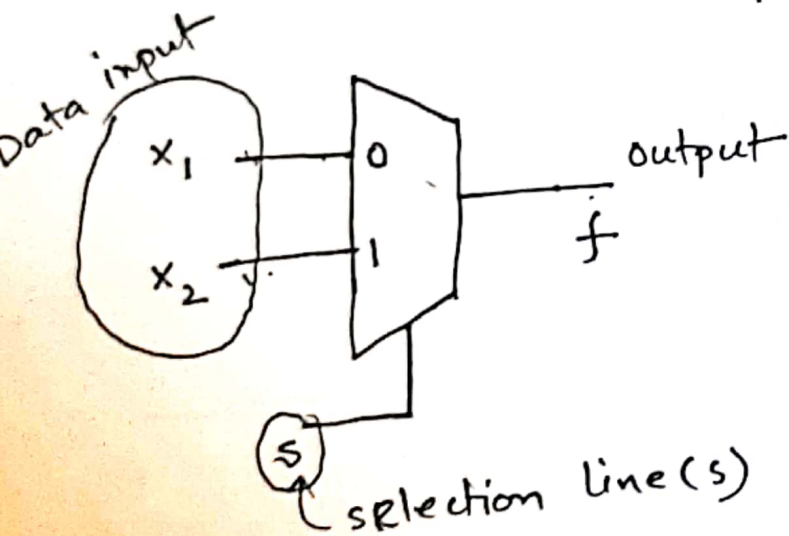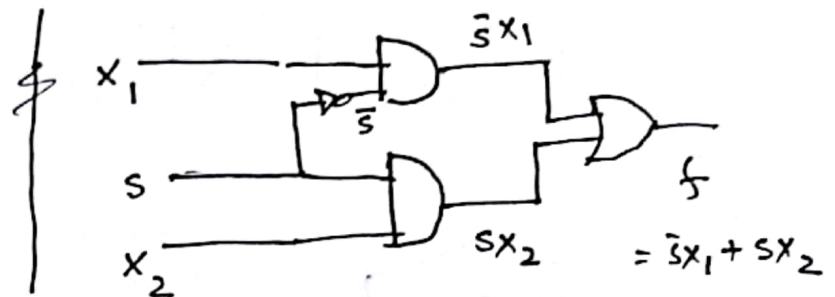
$$\begin{aligned} f &= \bar{s}x_1\bar{x}_2 + \bar{s}x_1x_2 + s\bar{x}_1x_2 + sx_1x_2 \\ &= \bar{s}x_1(\bar{x}_2 + x_2) + sx_2(\bar{x}_1 + x_1) \\ &= \bar{s}x_1 + sx_2 \end{aligned}$$


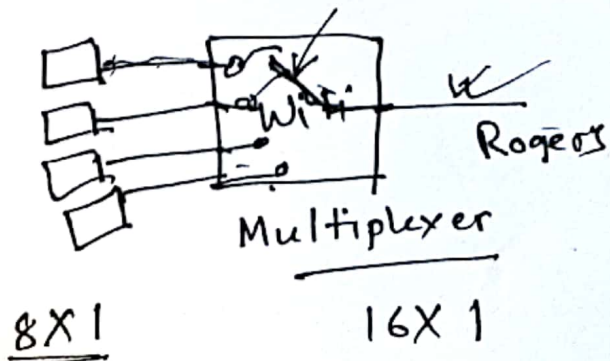
## Multiplexer



- $2^n \rightarrow$  input
- $(n) \rightarrow$  selection line
- $1 \rightarrow$  output

$$\begin{aligned} n &\rightarrow 1 & \underline{\underline{2 \times 1}} \\ 2^1 &\rightarrow 2 \\ n &\rightarrow 2 & \underline{\underline{4 \times 1}} \\ 2^2 &\rightarrow 4 \end{aligned}$$






(2)

Selection		data i/p	
$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

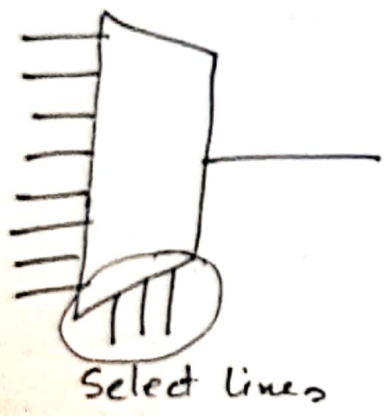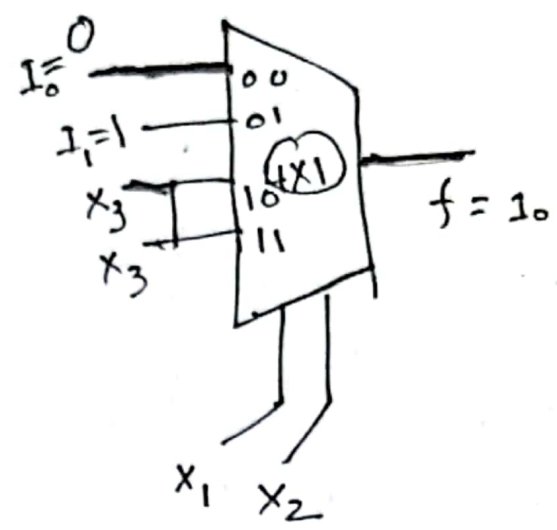



# Implementation Technology

(3)

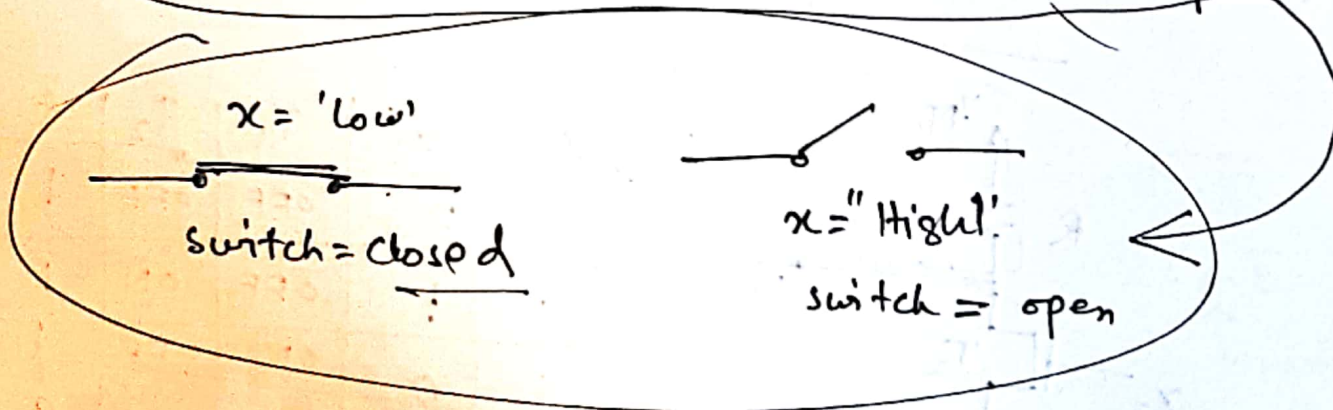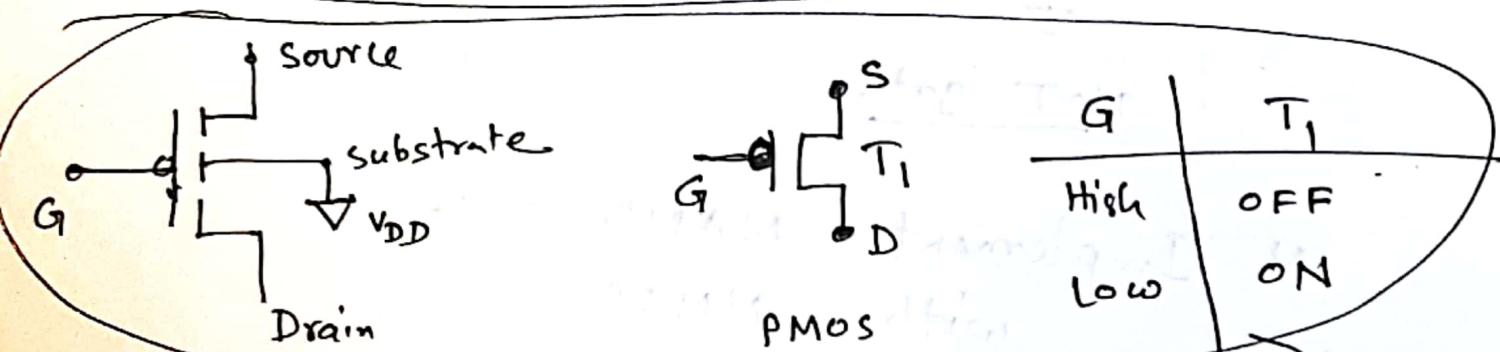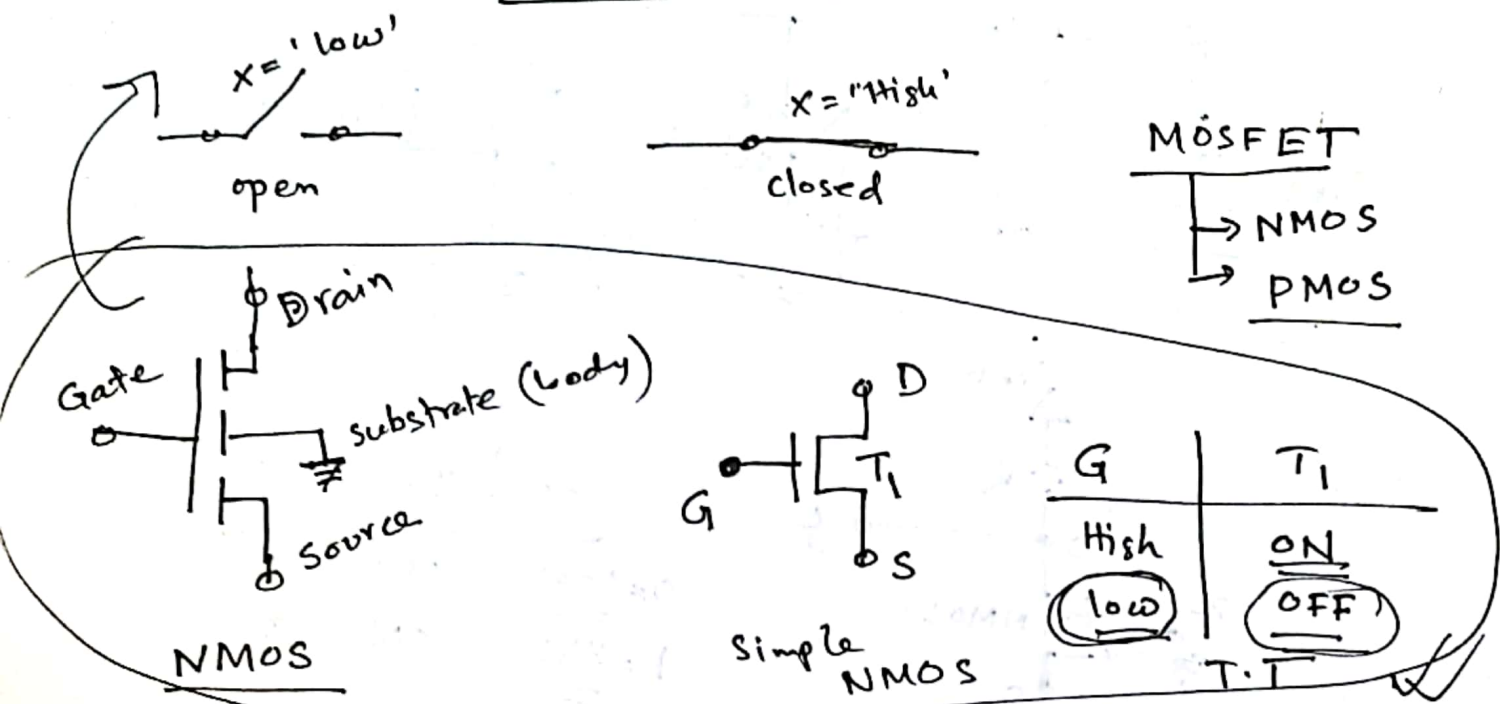




(4)

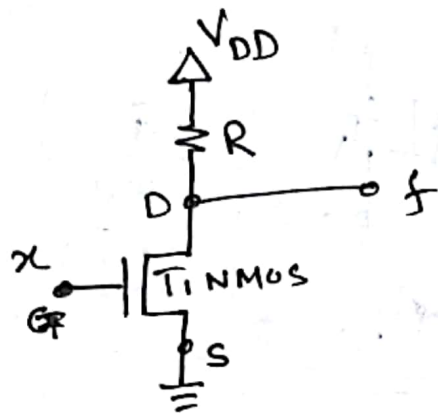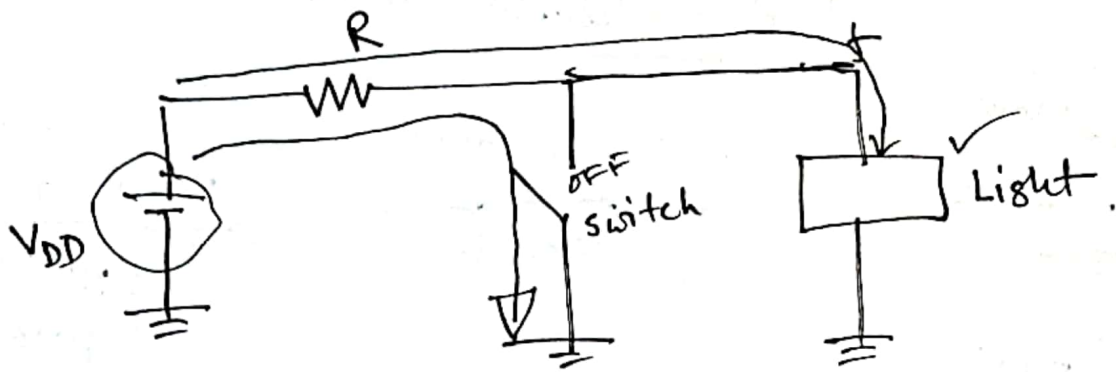
NOT gate

$x$	$T_1$	$f$
0 = Low	OFF	1
1 = High	ON	0



Implement NAND gate with NMOS

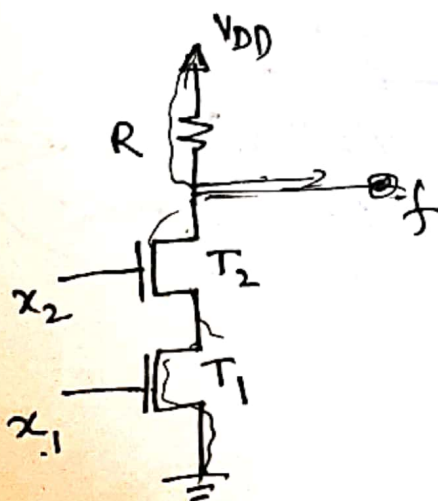

$x_1$	$x_2$	$T_1$	$T_2$	$f$
0	0	OFF	OFF	1
0	1	OFF	ON	1
1	0	ON	OFF	1
1	1	ON	ON	0

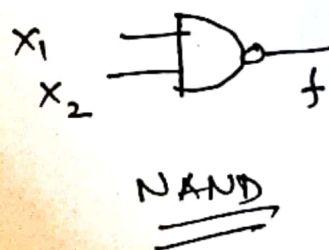


$x_1$	$x_2$	$f$
0	0	1
0	1	1
1	0	1
1	1	0

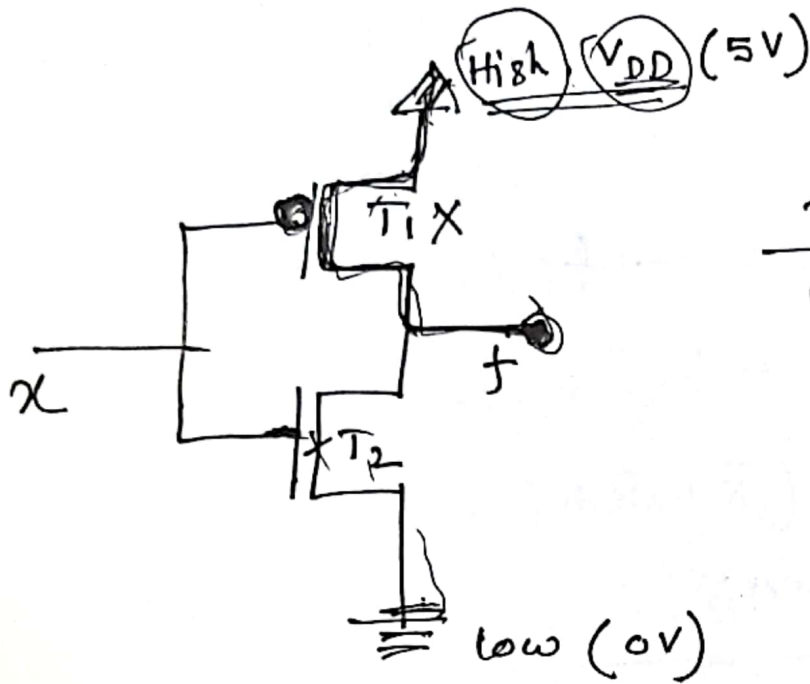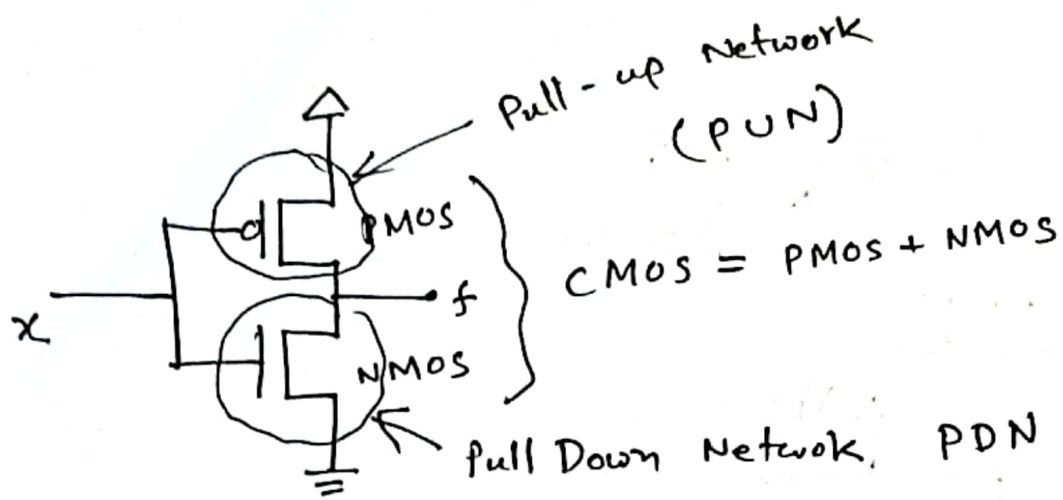

$x$	$T_1$ (PMOS)	$T_2$ (NMOS)	$f$
0	ON	OFF	1
1	OFF	ON	0



Implement NAND gate with CMOS

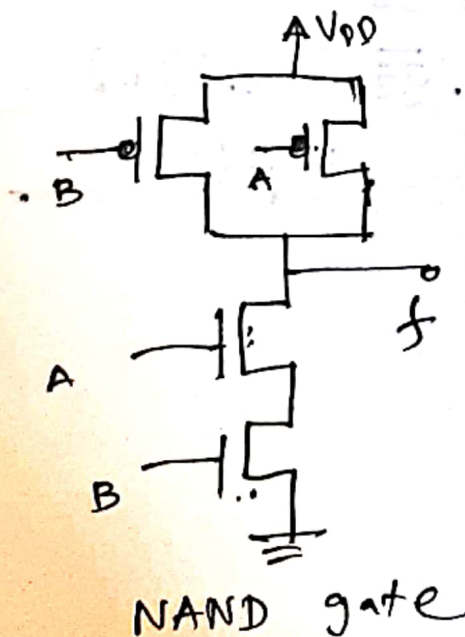

How to design PUN ✓

$$f = \overline{A \cdot B}$$

$$= \overline{A} + \overline{B}$$

↑ parallel

How to design PDN ✓

$$\overline{f} = \overline{\overline{A \cdot B}} = A \cdot B$$


↑ series

$$f = \bar{x} + \bar{y} \bar{z}$$

↑                      ↑  
series

6


PUN

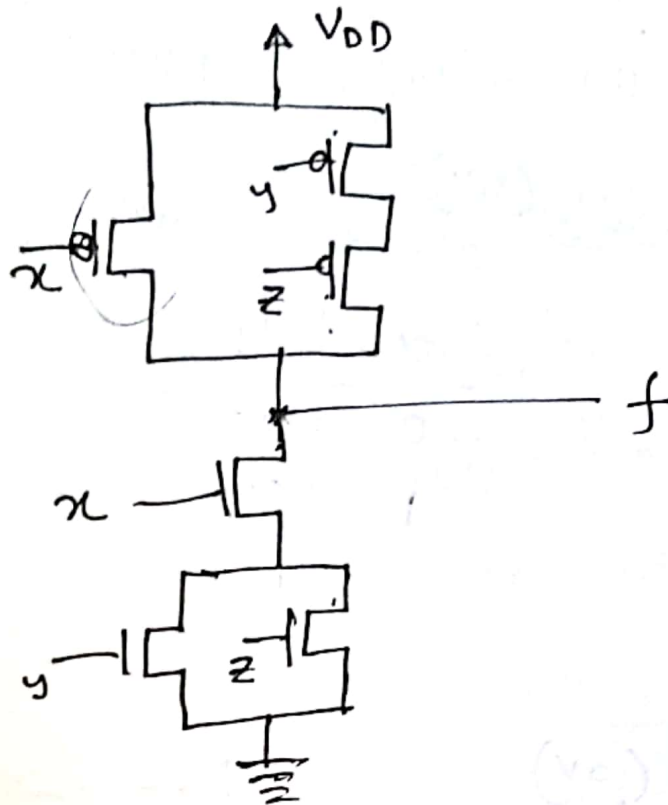


PDN
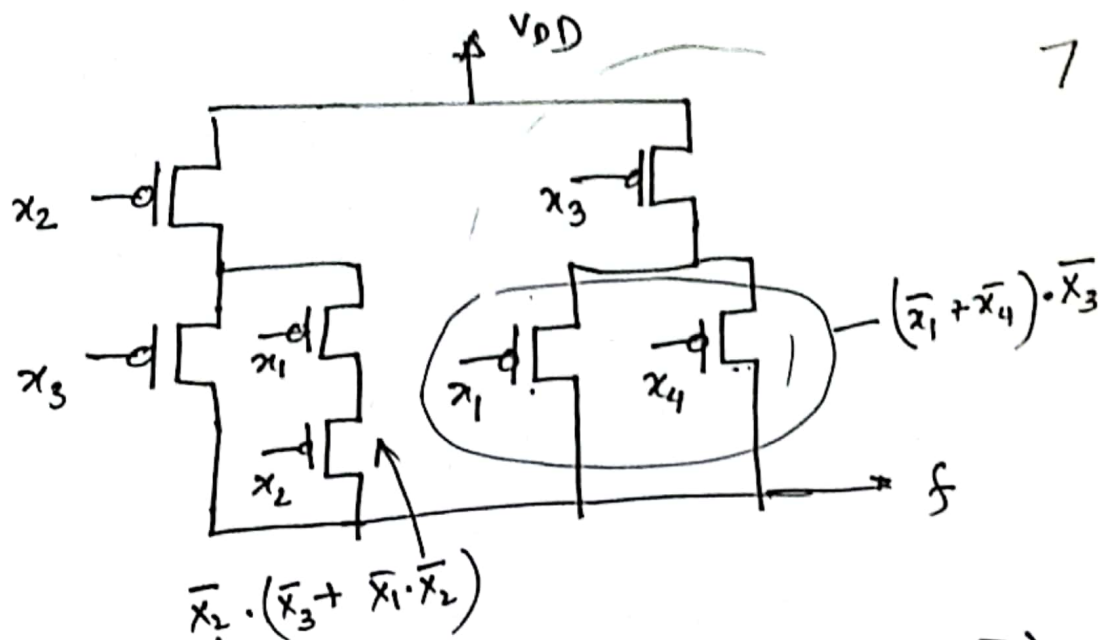
$$\begin{aligned} f &= \overline{\bar{x} + \bar{y} \bar{z}} \\ &= \bar{\bar{x}} \cdot \bar{\bar{y} \bar{z}} = x \cdot (\bar{\bar{y}} + \bar{\bar{z}}) \\ &= \underline{x(y + z)} \end{aligned}$$





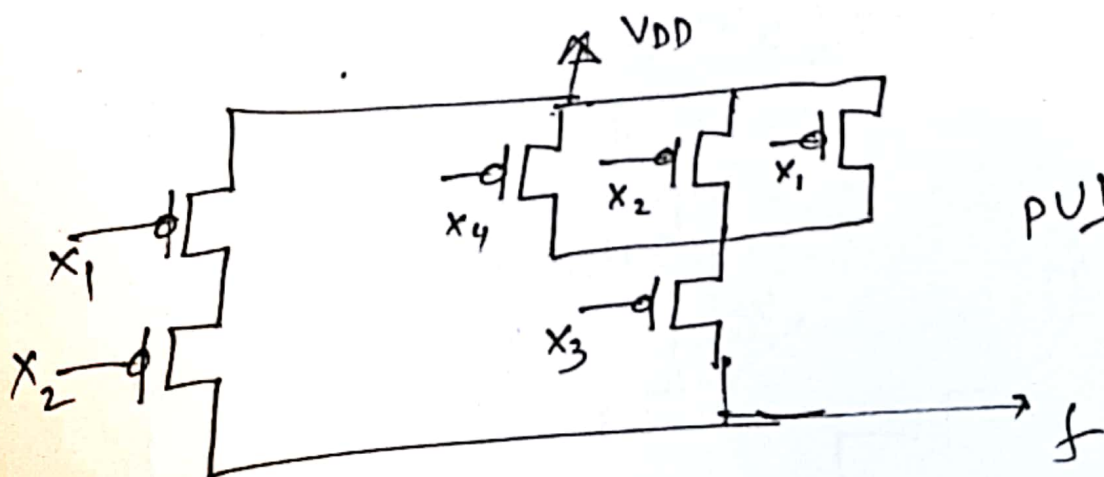
$$\begin{aligned}
 f &= (\bar{x}_1 + \bar{x}_4) \cdot \bar{x}_3 + \bar{x}_2 \cdot (\bar{x}_3 + \bar{x}_1 \cdot \bar{x}_2) \\
 &= \bar{x}_1 \cdot \bar{x}_3 + \bar{x}_3 \cdot \bar{x}_4 + \bar{x}_2 \cdot \bar{x}_3 + \bar{x}_1 \cdot \bar{x}_2 \\
 &= \bar{x}_3 (\bar{x}_1 + \bar{x}_4 + \bar{x}_2) + \bar{x}_1 \cdot \bar{x}_2
 \end{aligned}$$




PUN

$$\begin{aligned}
 \bar{f} &= \overline{\bar{x}_3 (\bar{x}_1 + \bar{x}_2 + \bar{x}_4) + \bar{x}_1 \cdot \bar{x}_2} \\
 &= \overline{\bar{x}_3 (\bar{x}_1 + \bar{x}_2 + \bar{x}_4)} \cdot \overline{\bar{x}_1 \cdot \bar{x}_2} \\
 &= [\overline{\bar{x}_3} + \overline{(\bar{x}_1 + \bar{x}_2 + \bar{x}_4)}] \cdot (\bar{x}_1 + \bar{x}_2) \\
 &= [x_3 + (\bar{x}_1 \cdot \bar{x}_2 \cdot \bar{x}_4)] \cdot (x_1 + x_2) \\
 \bar{f} &= [x_3 + (x_1 x_2 x_4)] \cdot \underline{\underline{(x_1 + x_2)}}
 \end{aligned}$$


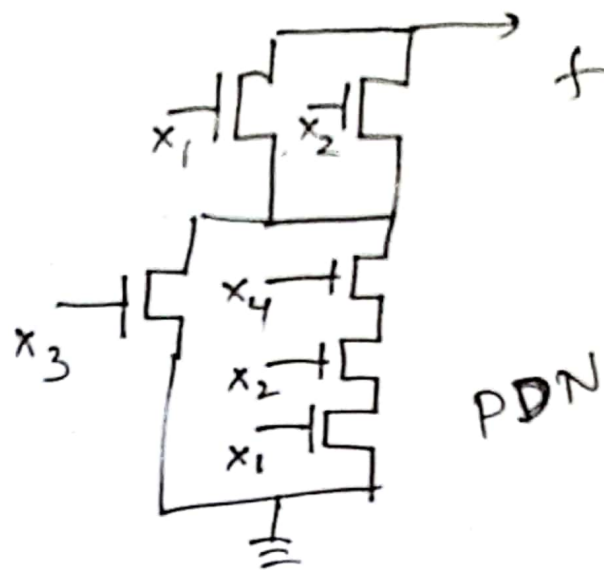


$$F = \underline{\underline{x + yz}}$$
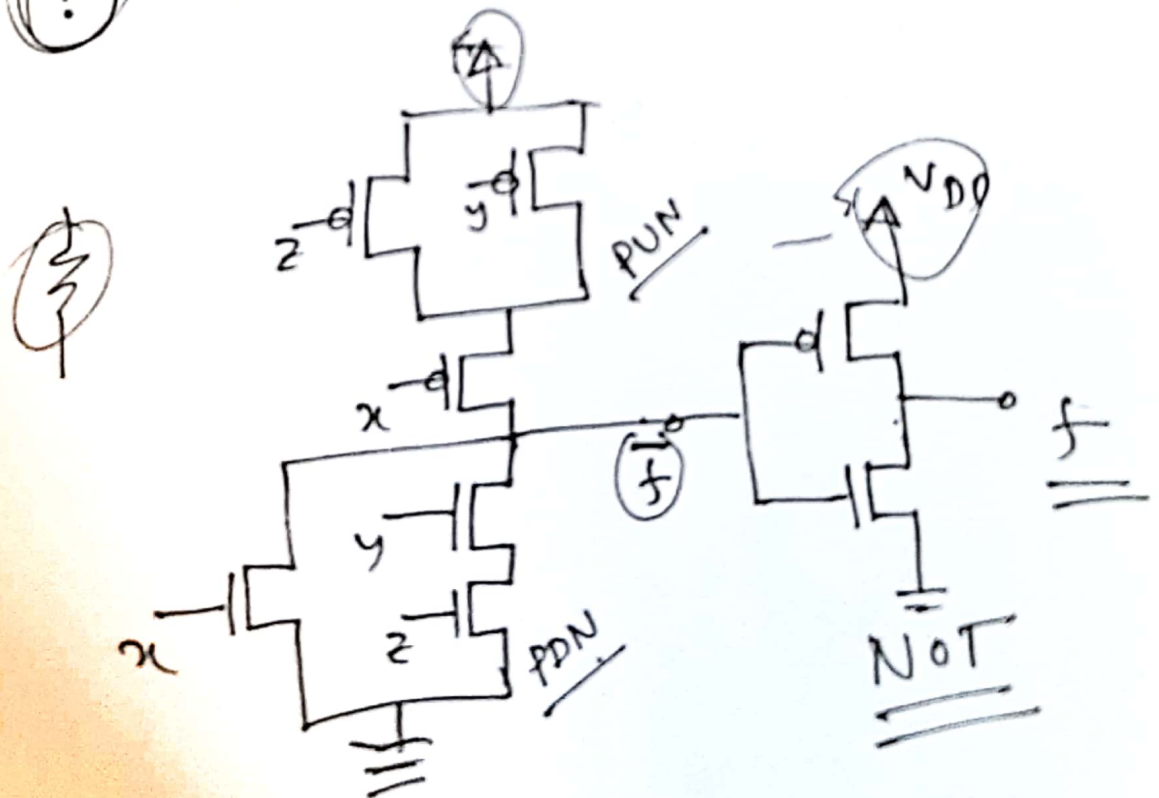
$$\overline{F} = \overline{x + yz} = \overline{x} \cdot (\overline{yz}) = \overline{x} \cdot (\overline{y} + \overline{z})$$











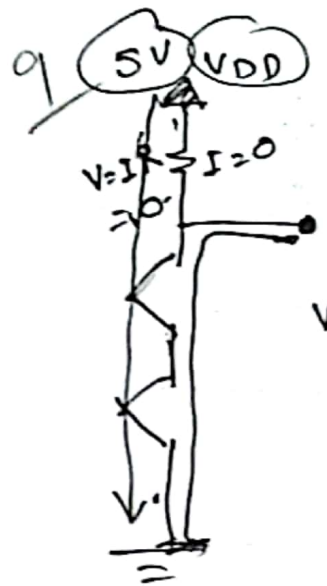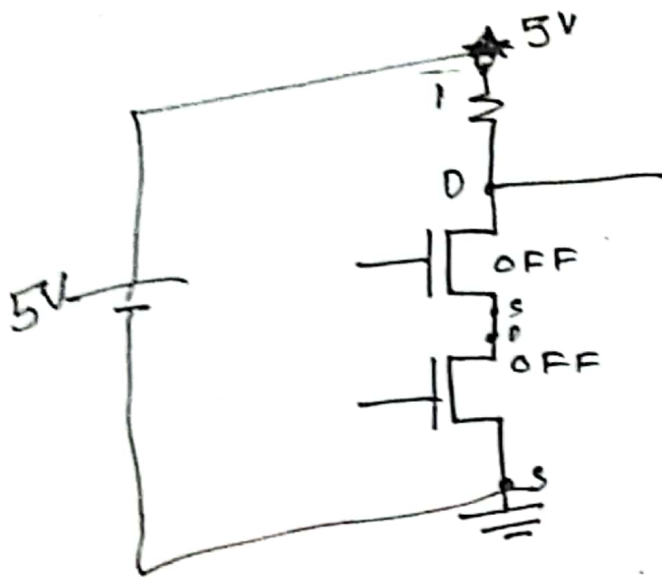

$$V_f + 0 = V_{DD}$$
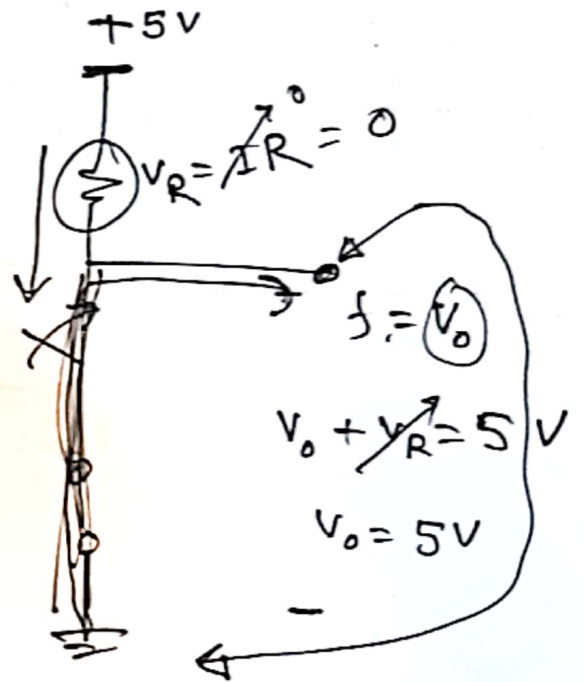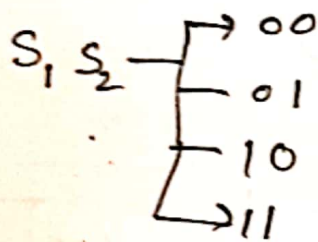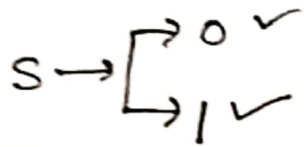
$$V_f = \underline{\underline{V_{DD} = 1V}}$$



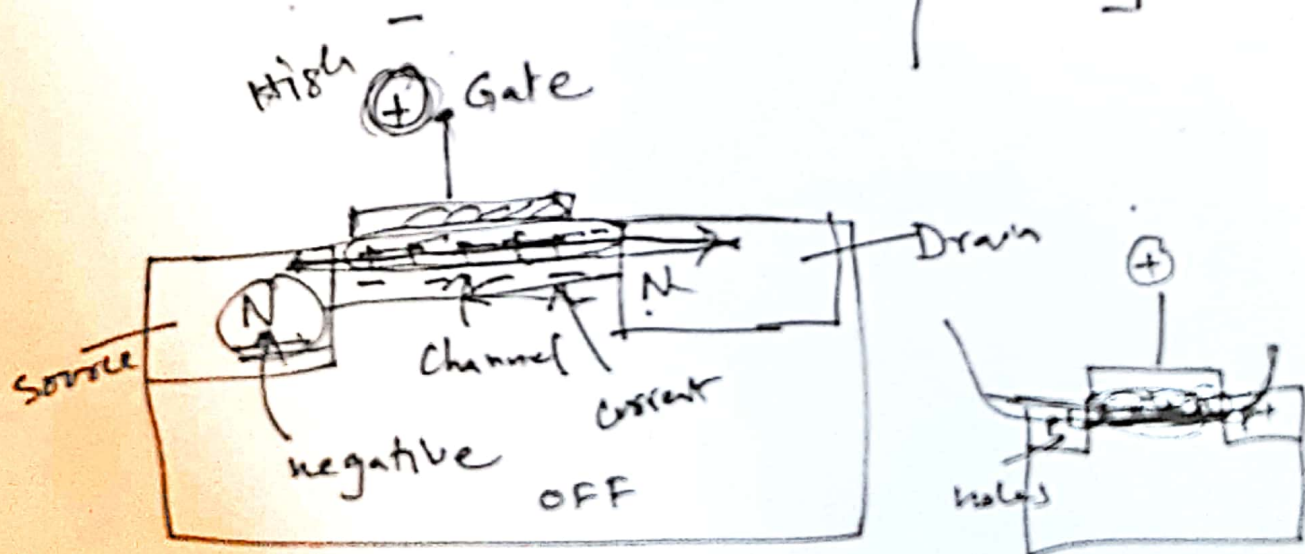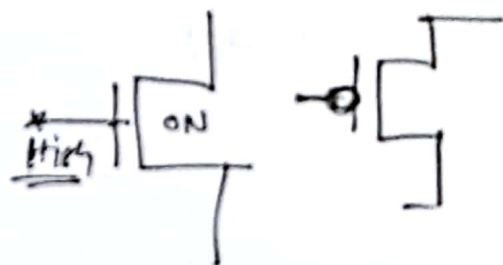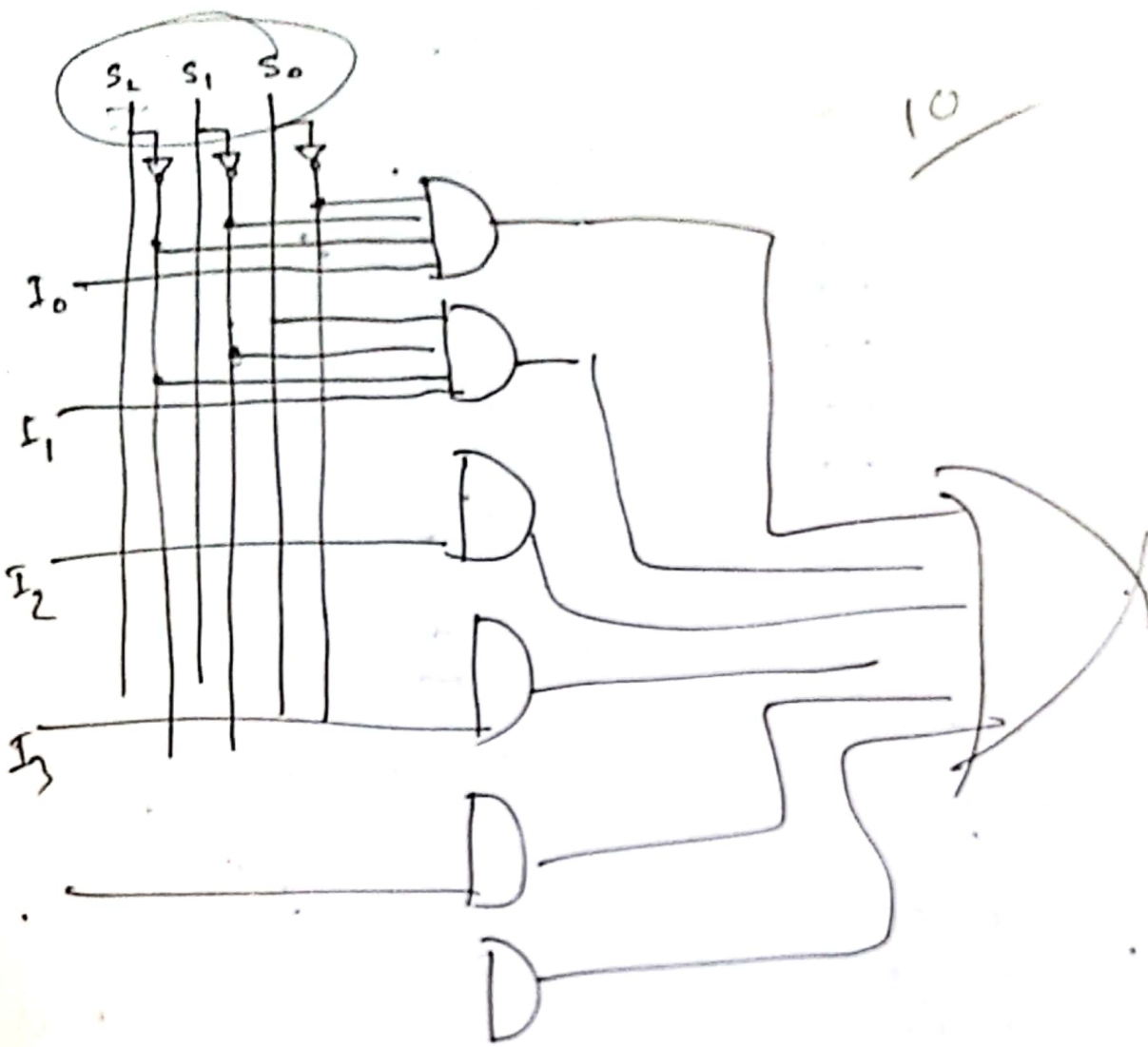

(11)

